

## 45W USB Type-C™ PD adapter board with controllers STCH03 QR flyback, SRK1001 adaptive synchronous rectifier and STUSB4761 USB Type-C™ PD

### Introduction

This application note describes the operation and the performance of the [EVLSTCH03-45WPD](#) demo board.

The EVLSTCH03-45WPD is designed to deliver a maximum output current of 3 A and a variable output voltage between 5 V and 20 V. The maximum power that the EVLSTCH03-45WPD demo board can deliver is 45 W.


The EVLSTCH03-45WPD is based on the quasi-resonant flyback controller [STCH03](#), the synchronous rectifier controller [SRK1001](#), and the USB-PD Type-C controller [STUSB4761](#).

The EVLSTCH03-45WPD 45W USB Type-C Power Delivery 3.0 adapter is a USB-IF certified solution and reference design, the respective Test ID reference are:

- Power Brick EVLSTCH03-45WPD TID: 2071
- PD Controller STUSB4761 TID: 2070



Figure 1. EVLSTCH03-45WPD evaluation board

 

#### Important:

*This product is intended for evaluation purpose only. Although it is designed to satisfy safety isolation requirement it shall be operated in a designated test area by personnel qualified and all testing should be performed with an isolation transformer to provide the AC input to the demo board.*


## 1 Introduction chapter 1

This application note describes how to design a 45 W Type-C Power Delivery adapter solution that supports the following PDOs: 5 V / 3 A, 9 V / 3 A, 12 V / 3 A, 15 V / 3 A, 20 V / 2.25 A and accepts a wide inputs main range (90 V<sub>AC</sub> to 265 V<sub>AC</sub>).

The EVLSTCH03-45WPD represents an effective solution where isolation from the AC mains is required, and where cost effectiveness, high efficiency and low standby power are essential.

The EVLSTCH03-45WPD is an isolated power supply developed for USB Type-C Power Delivery adapter applications. The primary side of the evaluation board implements a Quasi Resonant flyback converter based on an STCH03 controller with optocoupler feedback for the voltage regulation. The secondary side implements an Adaptive Synchronous Rectification based on the SRK1001 controller in order to increase the overall efficiency of the system. The management of the USB Type-C Power delivery is based on an STUSB4761 controller. [Figure 2](#) below shows the block diagram of the demo board.

**Figure 2. EVLSTCH03-45WPD evaluation board block diagram**

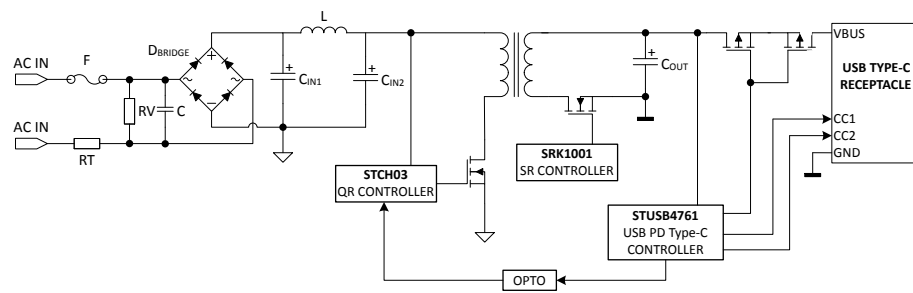

The features of the three controllers used to realize this adapter allow a compact and lightweight design with high power density and with very low stand-by consumption, below 30 mW.

This evaluation board is compliant with CoC Tier 2 regulations thanks to the new MDmesh M6 technology primary Power MOSFET [STF7N65M6](#) and new STripFET F7 technology and synchronous Power MOSFET [STL110N10F7](#) that offer a very low on-state resistance.

The EVLSTCH03-45WPD is protected against destructive electrostatic discharge from the USB Type-C connector using a Dual Transil array for ESD protection, [ESDA25L](#).

## 2 Specifications

Table 1 shows the specifications of the demonstration board. This design could be used to develop a charger/adaptor and the circuit board would need to be modified depending on shape and form factor of the housing. Performance should be evaluated with the new design and layout/components adjusted to meet the target specification.


**Table 1. EVLSTCH03-45WPD evaluation board specifications**

| Parameter                     | Symbol        | Value   |
|-------------------------------|---------------|---|
| AC mains input voltage        | $V_{IN}$      | 90 V <sub>AC</sub> up to 265 V <sub>AC</sub>                |
| AC mains frequency            | $f_{IN}$      | 47 Hz to 63 Hz  |
| Nominal output current        | $I_{OUT-NOM}$ | 3 A, at 5 V / 12 V / 15 V; 2.25 A, at 20 V                  |
| Maximum output current        | $I_{OUT-MAX}$ | $I_{OUT-NOM} + 12.5\%$                                      |
| Maximum output power          | $P_{OUT-MAX}$ | 45 W  |
| Power Delivery Objects (PDOs) | $V_{OUT}$     | 5 V / 3 A, 9 V / 3 A, 12 V / 3 A, 15 V / 3 A, 20 V / 2.25 A |
| Maximum efficiency            | $\eta$        | > 90%, at $P_{OUT-MAX}$                                     |
| No-load input power           | $P_{NO-LOAD}$ | < 30 mW, at $V_{OUT} = 5 V$ and no cable plug in            |
| Power density                 | P/V           | 0.48 W/cm <sup>3</sup>                                      |
| Ambient temperature           | $T_{AMB}$     | 0°C up to 40 °C, free convection                            |
| Dimension                     | L x W x H     | 70 mm x 50 mm x 26.8 mm                                     |
| Conducted EMI                 | EMI           | EN55022 - Class B   |
| Energy efficiency             | -             | Meeting all DOE and UE CoC requirements                     |
| Safety                        | -             | EN60065   |
| RoHS                          | -             | Compliant   |

### 3 Schematic

The circuit diagram of the EVLSTCH03-45WPD evaluation board is shown in Figure 3.

**Figure 3. EVLSTCH03-45WPD evaluation board schematic**

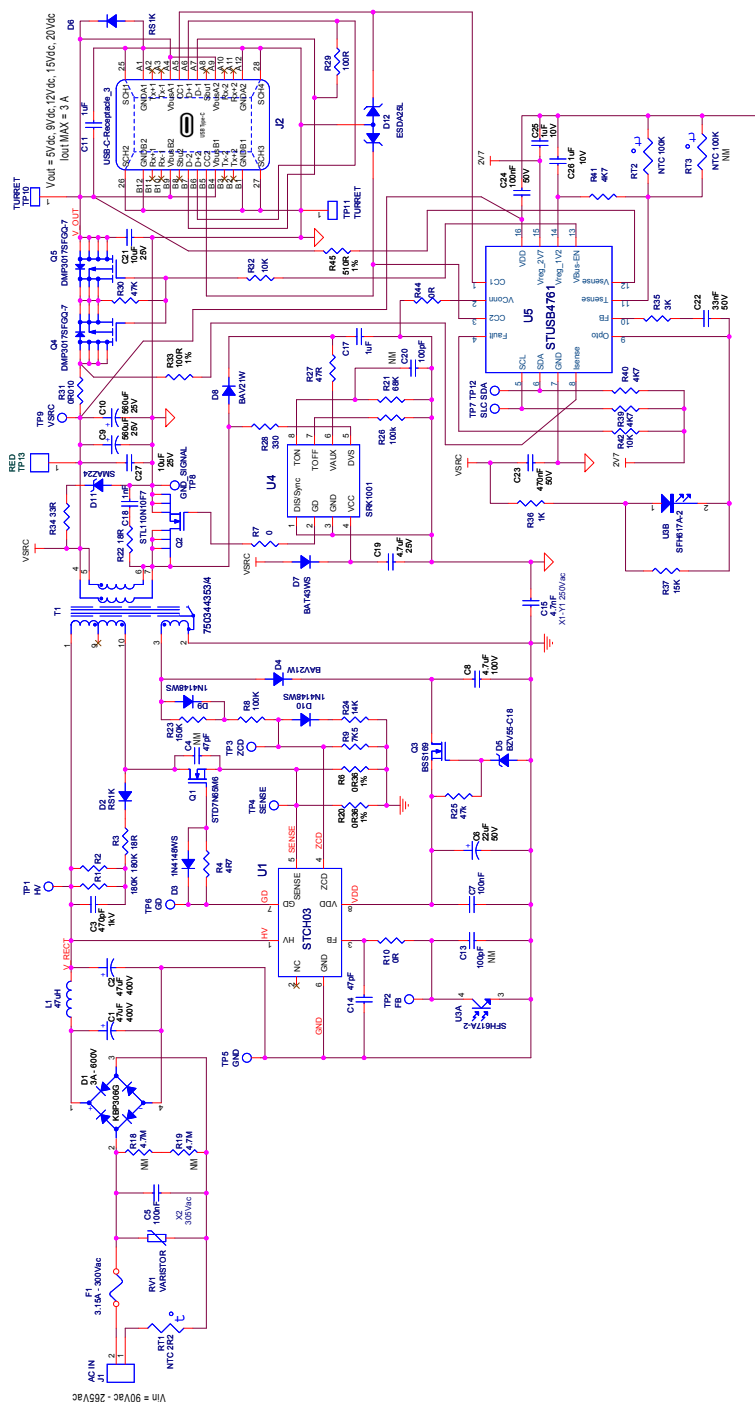



## 4 Bill of materials

**Table 2. EVLSTCH03-45WPD evaluation board bill of materials**

| Ref. | Part/Value            | Description                       | Manufacturer        |
|------|-----------------------|-----------------------------------|---------------------|
| C1   | 47uF–400V             | Aluminium Electrolytic            | Nippon Chemicon     |
| C2   | 47uF–400V             | Aluminium Electrolytic            | Nippon Chemicon     |
| C3   | 470pF–1kV             | Multilayer Ceramic X7R            | Murata              |
| C4   | Not mounted           | Capacitor                         | -                   |
| C5   | 0.1uF–305Vac          | EMI Suppression MKP               | TDK                 |
| C6   | 22uF–50V              | Aluminium Electrolytic            | Rubycon             |
| C7   | 0.1uF–50V             | Multilayer Ceramic X7R            | Kemet               |
| C8   | 4u7–100V              | Multilayer Ceramic X7R            | AVX                 |
| C9   | 560uF–25V             | Aluminium Conductive Polymer      | Kemet               |
| C10  | 560uF–25V             | Aluminium Conductive Polymer      | Kemet               |
| C11  | 1uF–50V               | Multilayer Ceramic X7R            | Samsung             |
| C13  | Not mounted           | Capacitor                         | -                   |
| C14  | Not mounted           | Capacitor                         | -                   |
| C15  | 4.7nF–250Vrms         | X1 Y1 Ceramic                     | Murata              |
| C17  | 1uF–50V               | Multilayer Ceramic X7R            | Samsung             |
| C18  | 1nF–2kV               | Multilayer Ceramic X7R            | Johansondielectrics |
| C19  | 4u7–25V               | Multilayer Ceramic X7R            | Kemet               |
| C20  | Not mounted           | Capacitor                         | -                   |
| C21  | 10uF–25V              | Multilayer Ceramic X7R            | Kemet               |
| C22  | 0.033uF–50V           | Multilayer Ceramic X7R            | Kemet               |
| C23  | 0.47uF–50V            | Multilayer Ceramic X7R            | AVX                 |
| C24  | 0.1uF–50v             | Multilayer Ceramic X7R            | Kemet               |
| C25  | 1uF–10V               | Multilayer Ceramic X7R            | Kemet               |
| C26  | 1uF–10V               | Multilayer Ceramic X7R            | Kemet               |
| C27  | 10uF–25V              | Multilayer Ceramic X7R            | Kemet               |
| D1   | 3A–600V               | Bridge Rectifier                  | Diodes              |
| D2   | RS1K / 1A–800V        | Fast Switching Rectifier          | Vishay              |
| D3   | 1N4148WS / 150mA–100V | Small Signal Fast Switching Diode | Fairchild           |
| D4   | BAV21W / 250mA–250V   | Small Signal Switching Diodes     | Vishay              |
| D5   | BZV55 / C18–500mW     | Zener Diode                       | Nexperia            |
| D6   | RS1K / 1A–800V        | Fast Switching Rectifier          | Vishay              |
| D7   | BAT43WS / 200mA–30V   | Schottky Diode                    | Diodes              |
| D8   | BAV21W / 250mA–250V   | Switching Diode                   | Diodes              |
| D9   | 1N4148WS / 150mA–100V | Signal Diode                      | Fairchild           |
| D10  | 1N4148WS / 150mA–100V | Signal Diode                      | Fairchild           |
| D11  | SMAZ24 / 1W           | Zener Diode                       | Diodes              |
| D12  | ESDAL / 10mA–1.2V     | Dual Transil                      | STMicroelectronics  |


| Ref. | Part/Value             | Description                    | Manufacturer       |
|------|------------------------|--------------------------------|--------------------|
| F1   | 3.15A–300Vac           | Time-Delay Fuses               | Copper Bussmann    |
| J1   | 20A–300Vac             | PCB Header Male/Female         | WÜrth Electronics  |
| J2   | 1054500101             | Connector USB 3.1, type C, 90° | MOLEX              |
| L1   | 47uH–1.8A              | Fixed Inductor                 | WÜrth Electronics  |
| Q1   | STD7N65M6 / 0.91Ω–650V | Power Mosfet                   | STMicroelectronics |
| Q2   | STL110N10F7 / 6mΩ–100V | Power Mosfet                   | STMicroelectronics |
| Q3   | BSS169 / 12Ω–100V      | Power Mosfet                   | Infineon           |
| Q4   | DMP3013SFV / 9.5mΩ–30V | Power Mosfet                   | Diodes             |
| Q5   | DMP3013SFV / 9.5mΩ–30V | Power Mosfet                   | Diodes             |
| RT1  | 2.2R–7A                | NTC                            | Epcos              |
| RT2  | 100K–100mW             | NTC                            | Vishay             |
| RT3  | Not mounted            | NTC                            | -                  |
| RV1  | 275Vac–25A             | SIOV metal oxide varistors     | Epcos              |
| R1   | 180k–0.5W              | Anti-Surge Thick Film Chip     | Panasonic          |
| R2   | 180k–0.5W              | Anti-Surge Thick Film Chip     | Panasonic          |
| R3   | 18R–0.5W               | Anti-Surge Thick Film Chip     | Panasonic          |
| R4   | 4R7–0.125W             | Thick Film Chip                | Vishay             |
| R6   | 0R36–0.5W              | Flat Chip                      | TE                 |
| R7   | 0R–0.0625W             | Thick Film Chip                | Vishay             |
| R8   | 100k–0.125W            | Thick Film Chip                | Yageo              |
| R9   | 7k5–0.125W             | Thick Film Chip                | Vishay             |
| R10  | 0R–0.0625W             | Thick Film Chip                | Vishay             |
| R18  | Not mounted            | Resistor                       | -                  |
| R19  | Not mounted            | Resistor                       | -                  |
| R20  | 0R36–0.5W              | Flat Chip                      | TE                 |
| R21  | 68k–0.0625W            | Thick Film Chip                | Vishay             |
| R22  | 18R–0.250W             | Thick Film Chip                | Vishay             |
| R23  | 150k–0.125W            | Thick Film Chip                | Vishay             |
| R24  | 14k–0.125W             | Thick Film Chip                | Vishay             |
| R25  | 47k–0.125W             | Thick Film Chip                | Yageo              |
| R26  | 100k–0.0625W           | Thick Film Chip                | Yageo              |
| R27  | 47R–0.0625W            | Thick Film Chip                | Vishay             |
| R28  | 330R–0.0625W           | Thick Film Chip                | Yageo              |
| R29  | 100R–0.0625W           | Thick Film Chip                | Yageo              |
| R30  | 47k–0.125W             | Thick Film Chip                | Vishay             |
| R31  | 0R010–0.750W           | Power Thick Film Chip          | SSM                |
| R32  | 10k–0.0625W            | Thick Film Chip                | Vishay             |
| R33  | 100R–0.250W            | Thick Film Chip                | Panasonic          |
| R34  | 33R–0.250W             | Thick Film Chip                | Yageo              |
| R35  | 3k–0.0625W             | Thick Film Chip                | Vishay             |

| Ref. | Part/Value     | Description                          | Manufacturer       |
|------|----------------|--------------------------------------|--------------------|
| R36  | 1k-0.0625W     | Thick Film Chip                      | Yageo              |
| R37  | 15k-0.0625W    | Thick Film Chip                      | Vishay             |
| R39  | 4k7-0.0625W    | Thick Film Chip                      | Vishay             |
| R40  | 4k7-0.0625W    | Thick Film Chip                      | Vishay             |
| R41  | 4.7k-0.0625W   | Thick Film Chip                      | Vishay             |
| R42  | 10k-0.0625W    | Thick Film Chip                      | Vishay             |
| R44  | 0R-0.125W      | Thick Film Chip                      | Vishay             |
| R45  | 510R-0.0625W   | Thick Film Chip                      | Yageo              |
| T1   | 750344353rev00 | Transformer                          | WÜrth Electronics  |
| U1   | STCH03         | Offline PWM controller               | STMicroelectronics |
| U3   | SFH617A-2      | Optocoupler                          | Vishay             |
| U4   | SRK1001        | Synchronous rectification controller | STMicroelectronics |
| U5   | STUSB4761      | USB PD Type-C controller             | STMicroelectronics |


## 5 PCB layout

The PCB layout top side and bottom side of the EVLSTCH03-45WPD evaluation board are shown in [Figure 4](#) and [Figure 5](#) respectively. The PCB uses a two-layer technology in FR4 material with copper thickness of 70  $\mu\text{m}$ .

**Figure 4. EVLSTCH03-45WPD PCB top layer layout**

 

**Figure 5. EVLSTCH03-45WPD PCB bottom layer layout**

 


## 6 Board description

The EVLSTCH03-45WPD is an evaluation board based on the quasi-resonant flyback controller STCH03, the synchronous rectifier controller SRK1001, and the USB Power Delivery controller STUSB4761. [Figure 6](#) and [Figure 7](#) below show the top and bottom views of the demo board respectively.

**Figure 6. EVLSTCH03-45WPD top view**



**Figure 7. EVLSTCH03-45WPD bottom view**

 

### 6.1 Input stage and filtering

Fuse F1 provides protection from component failure and isolates the circuit from AC mains when a fault occurs. NTC thermistor RT1 is used to limit inrush current at start-up when the adapter is connected to AC mains. Varistor RV1 provides overvoltage protection due to voltage spikes and transient from AC mains. Capacitor C5 provides differential mode noise filtering for EMI attenuation. Bridge rectifier D1 rectifies the AC line voltage and provides a full wave rectified DC across C1 and C2. Inductor coil L1 placed between C1 and C2 allows to reduce the residual AC ripples present in the rectified DC. PI filter improves EMI performance.

### 6.2 Flyback controller and primary MOSFET

The STCH03 is a quasi-resonant flyback controller with HV start-up cell and a high performance low voltage PWM controller chip in the same package that minimizes power consumption.

This PWM controller turns on the primary MOSFET to allow energy to be stored inside the primary winding of the flyback transformer during the ON time. After the primary MOSFET turn-off, the energy is electromagnetically transferred to the secondary winding of the flyback transformer and hence to the secondary side capacitors and load.

CV regulation loop is achieved by secondary side feedback, the output voltage information is transferred via an optocoupler on the FB pin of the STCH03 to get the selected output voltage. The capacitor C14 on the FB pin and internal equivalent resistance of the pin  $R_{FB}$  provide a high frequency pole, while the loop compensation is done at secondary side by C22 and R35 connected to the CV regulator of the STUSB4761 controller.

CC regulation loop is fully integrated into the IC, R6 - R20 resistors set the primary side regulation current level and sense the current flowing on the primary MOSFET to implement the overcurrent protection (OCP).

To sense the transformer demagnetization, the ZCD pin is connected through a voltage divider (R23 // D9 + R8 – R9 // [R24 + D10]) to an auxiliary winding of the flyback transformer. The controller uses this pin to detect the zero-crossing signal for proper quasi-resonant operations and output voltage protection OVP and UVP.

For more detailed information on STCH03 operation and features, please refer to the datasheet (1).


The Power MOSFET Q1 is a DPAK N-channel 650 V MDmesh M6 technology with  $R_{DS(ON)} = 0.99 \Omega$ . This new technology ensures a good compromise between low conduction losses and switching characteristics.

Described in the following paragraphs is a step-by-step design procedure of a quasi-resonant flyback converter for USB Type-C Power Delivery application based on STCH03 offline PWM controller for low stand-by adapters starting from the basic configuration shown in [Figure 8](#).

In this kind of application, the output voltage can vary from 5 V to 20 V so, it is very important to make pre-design choices in order to define the appropriate turn ratio of the power transformer.

Once the breakdown voltage of the Power MOSFET to be used has been defined, typically 650 V or 800 V, the maximum output voltage must be used to set the right turns ratio of the power transformer. At this point, using the maximum value of the current that can be delivered by the adapter and the turns ratio of the transformer, it is possible to define the other parameters as current sense resistor  $R_{SENSE}$ , zero current sense resistor  $R_{ZCD}$ , undervoltage sense resistor  $R_{UVP}$  and overvoltage sense resistor  $R_{OVP}$ .


Figure 8. STCH03 configuration basic

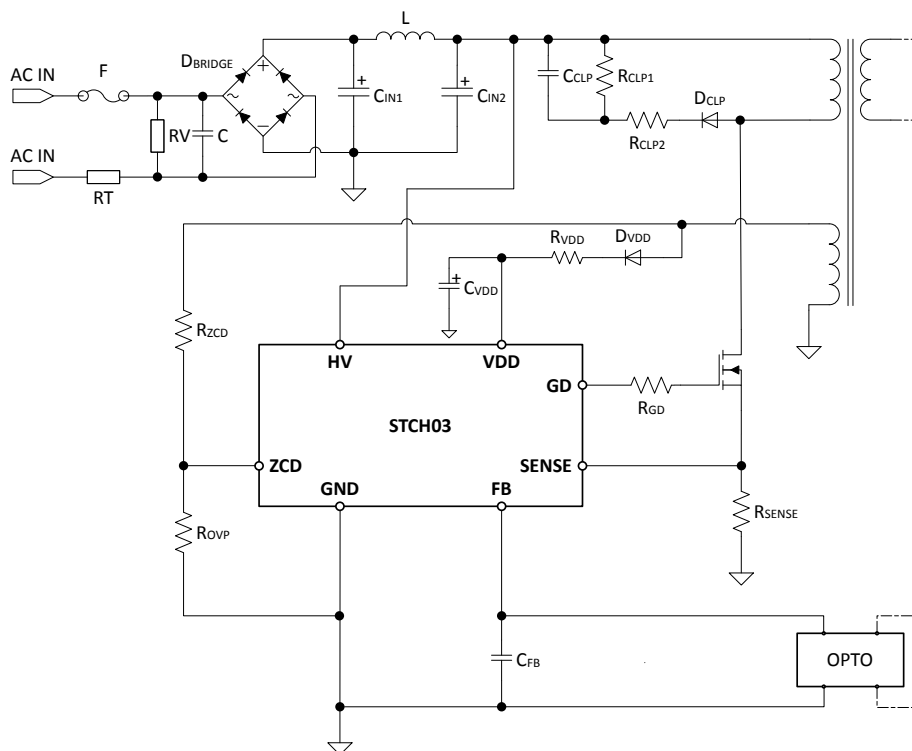

### 6.2.1 Power MOSFET selection

The design of the transformer and in particular the value of the reflected voltage depends on the choice of the breakdown voltage of the Power MOSFET. In fact, the sum of the maximum input voltage, reflected voltage and overvoltage spike, due to the leakage inductance, must be lower than the breakdown of the internal Power MOSFET. It is mandatory to add some margin, typically 10% ÷ 30% more, to cover the possible overvoltage present in the main line. Figure 9 illustrates schematically how the drain voltage is composed.

**Figure 9. Voltage between drain and source of the Power MOSFET,  $V_{DS}$**

 

The maximum voltage on the Power MOSFET drain is given by the following equation:

**Equation 1**

$$V_{DSMAX} = V_{INMAX} + V_{REFLECTED} + V_{SPIKE} + V_{MARGIN}$$

(1)

It is possible to derive the reflected voltage as

**Equation 2**

$$V_{REFLECTED} = V_{DSMAX} - V_{INMAX} - V_{SPIKE} - V_{MARGIN}$$

(2)

### 6.2.2 Turns ratio transformer selection

Once the reflected voltage is defined, it is possible to define the turns ratio of the transformer by the following equation:

**Equation 3**

$$n = \frac{N_{PRI}}{N_{SEC}} = \frac{V_{REFLECTED}}{V_{OUT}}$$

(3)

Where  $N_{PRI}$  is the number of the primary side windings,  $N_{SEC}$  is the number of secondary side windings,  $V_{REFLECTED}$  is the reflected voltage given by Equation 3 and finally  $V_{OUT}$  is the maximum output voltage of the adapter.

### 6.2.3 Current sense resistor selection

The STCH03 primary side controller is equipped with the current primary side regulation and therefore it is very important to choose the right current regulation level that allows the management of the output current to the STUSB4761 secondary side controller. The output overcurrent protection is effective when measured current overcomes the maximum output current  $I_{OUT\_MAX}$ . A good margin is to set the current primary side regulation level above 5% of the maximum output current  $I_{OUT\_MAX}$  and this threshold depends only by the turns ratio of the transformer according to the following equation:

**Equation 4**

(4)

$$I_{PSR} = \frac{N_{PRI}}{N_{SEC}} \frac{K_I}{2R_{SENSE}}$$

It is possible to derive the current sense resistor as:

**Equation 5**

(5)

$$R_{SENSE} = \frac{N_{PRI}}{N_{SEC}} \frac{K_I}{2I_{PSR}} = \frac{N_{PRI}}{N_{SEC}} \frac{K_I}{2I_{OUT - MAX}(1 + 5/100)}$$

**6.2.4**
**Zero current resistor selection**

ZCD pin functions are transformer demagnetization sensing for quasi-resonant operation, input/output voltage monitor and feedforward compensation.

The  $R_{ZCD}$  resistor can be calculated as follows:

**Equation 6**

(6)

$$R_{ZCD} = \frac{N_{AUX}}{N_{PRI}} \frac{L_{PR} R_{FF}}{T_D R_{SENSE}}$$

The value of the resistor depends on the turns ratio between auxiliary and primary windings, the value of the primary inductance and the value of the sense resistor  $R_{SENSE}$ . The other parameters are noted and available in the technical datasheet. It's recommended to split the value of  $R_{ZCD}$ , to improve the demagnetization sensing and the trigger for switching on of the Power MOSFET in Equation 7 and shown in Figure 10.

**Equation 7**

(7)

$$R_{ZCD} = R_{ZCD - 1} + R_{ZCD - 2}$$

The constraint is to use a resistance value for  $R_{ZCD-2}$  lower than 120 kΩ.


**Equation 8**

(8)

$$R_{ZCD - 2} \leq 120 \text{ k}\Omega$$



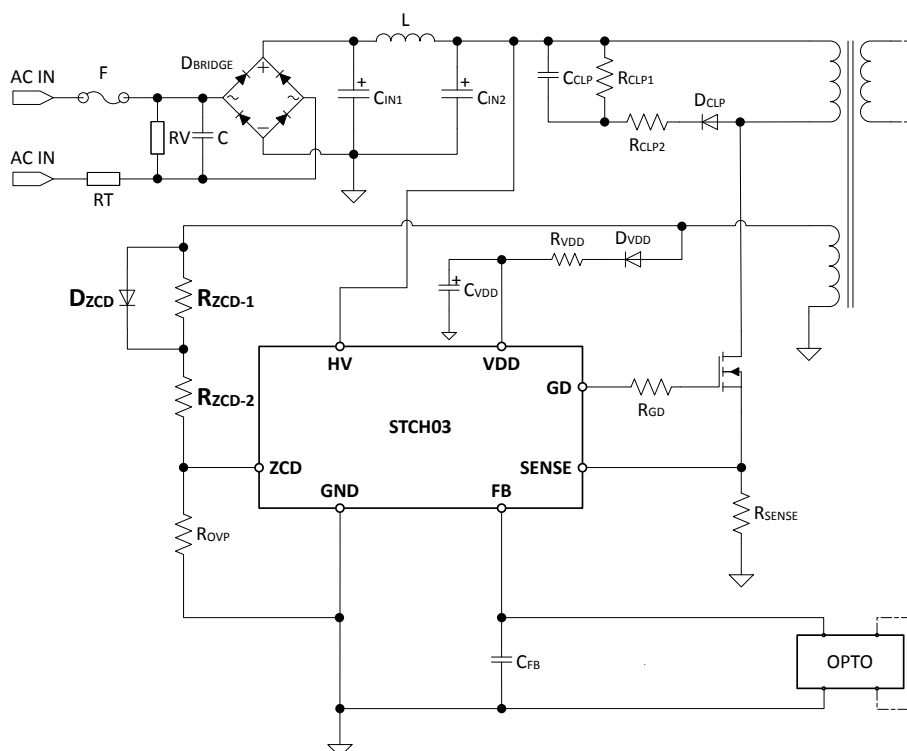
### Figure 10. Splitting of the $R_{ZCD}$ resistor



In this way, the phase relative to the feedforward compensation is separated from the triggering and output voltage monitoring. Figure 11 shows the two different phases.

### Figure 11. ZCD operational phases

 

When the primary Power MOSFET is in the ON state, the  $D_{ZCD}$  diode is open and the equivalent resistance is given by  $R_{ZCD-1}$  plus  $R_{ZCD-2}$ , line feedforward function continues to work properly and the current limitation does not depend on the input line voltage. While when the primary Power MOSFET is in an OFF state the  $D_{ZCD}$  diode is a short-circuit and the equivalent resistance is only  $R_{ZCD-2}$ . In this phase the ZCD pin senses the transformer demagnetization for quasi-resonant operation and a negative going edge triggers the Power MOSFET turn-on, furthermore the output voltage is monitored to realize the undervoltage and overvoltage protections.

### 6.2.5

#### UVP – OVP resistor selection

After the demagnetization of the transformer the voltage on the ZCD pin is sampled and held to get an accurate image of the output voltage to be used for overvoltage and undervoltage protection (OVP and UVP) sensing. OVP and UVP cannot be defined independently because they are in tracking. In order to avoid a conflict between the OVP and UVP thresholds and the output voltage range of the application, it is necessary to split the  $R_{OVP}$  resistance as shown in Figure 12.

As seen in Section 6.2.4 during this phase the diode  $D_{ZCD}$  is in conduction and the ZCD resistor is only  $R_{ZCD-2}$ . The  $D_{OVP}$  diode is open if the ZCD pin voltage is lower than the internal  $V_{UVP}$  threshold and the  $R_{UVP}$  resistor is chosen to set the level of UVP according to Equation 9.

#### Equation 9

(9)

$$R_{UVP} = \frac{\frac{N_{SEC}}{N_{AUX}} V_{UVP}}{V_{OUT - UVP} - \frac{N_{SEC}}{N_{AUX}} V_{UVP}} R_{ZCD-2}$$


Where  $V_{OUT-UVP}$  is the UVP desired threshold value,  $V_{UVP}$  is an internal parameter of the device,  $N_{AUX}$  is the number of the auxiliary windings,  $N_{SEC}$  is the number of secondary side windings and  $R_{ZCD-2}$  is defined by Equation 8.

The  $D_{OVP}$  diode is a short-circuit when the ZCD pin voltage is greater than the internal  $V_{OVP}$  threshold and therefore the  $R_{UVP}$  and  $R_{OVP}$  resistors are connected in parallel.  $R_{OVP}$  resistor is chosen to set the level of OVP according to Equation 10.

**Equation 10**

(10)

$$R_{OVP} = \frac{\frac{V_{OVP}}{\frac{N_{AUX}}{N_{SEC}} V_{OUT} - V_{OVP} - V_{OVP}} R_{ZCD} - 2R_{UVP}}{R_{UVP} - \frac{V_{OVP}}{\frac{N_{AUX}}{N_{SEC}} V_{OUT} - V_{OVP} - V_{OVP}} R_{ZCD} - 2}$$

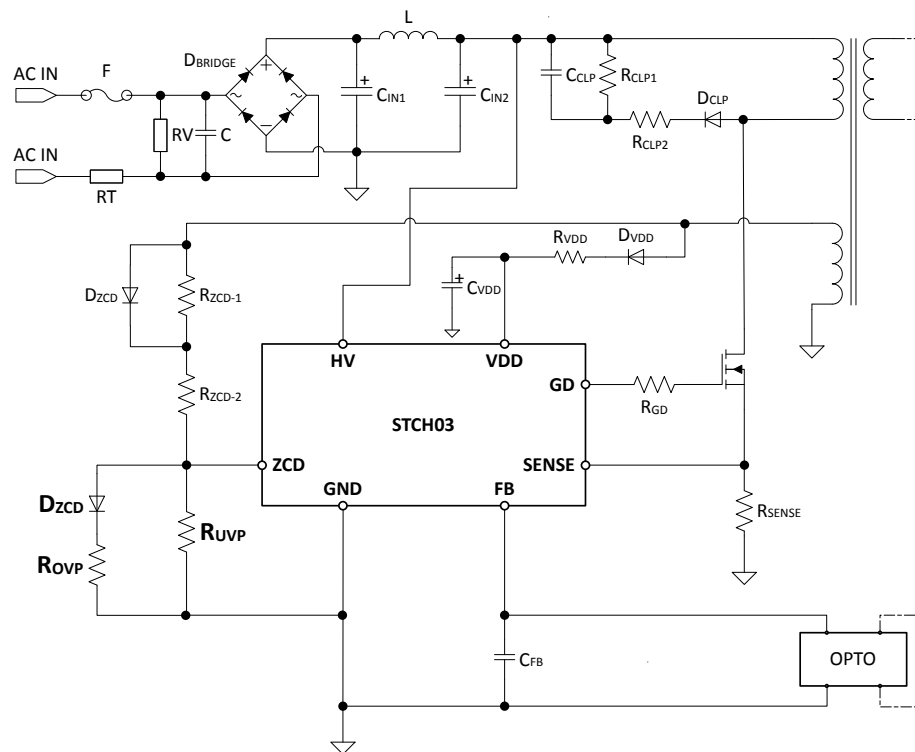**Figure 12. Splitting of the OVP and UVP threshold**


### 6.3 Snubber circuit


The capacitor C3, the resistor R1 // R2 and the diode D2 implement a snubber circuit to limit the leakage inductance voltage spike when the primary Power MOSFET is turned off. The clamping network ensures reliable power supply operation as it limits the maximum voltage on the primary Power MOSFET. The resistor R3 helps to reduce the residual ringing present across the primary Power MOSFET drain after the clamp action by damping the resonance oscillations between leakage inductance and equivalent drain capacitance at turn-off.

### 6.4 Transformer specification

The flyback transformer is designed in collaboration with Würth Elektronik and its reference part number is 750344353rev6A. Table 3 shows the transformer main parameters and Figure 13 shows the transformer schematic. For more details refer to the supplier spec sheet ([www.we-online.com](http://www.we-online.com)).

**Table 3. Transformer electrical specifications**

|                                  |                                      |
|----------------------------------|--------------------------------------|
| Manufacturer                     | Wurth Elektronik                     |
| Part number                      | 750344353rev6A                       |
| Core                             | RM8                                  |
| Type of insulation               | Reinforced                           |
| Coil former                      | Extended rail                        |
| Primary inductance               | 400 $\mu$ H $\pm$ 10%                |
| Saturation current               | 2 A, 20% roll-off from initial value |
| Leakage inductance               | 10 $\mu$ H max                       |
| Primary-to-secondary turns ratio | 7.5 : 1 $\pm$ 2%                     |
| Primary-to-auxiliary turns ratio | 3.21 : 1 $\pm$ 2%                    |

 **Figure 13. Transformer electrical diagram**


## 6.5

### Synchronous rectifier controller and secondary Power MOSFET

The SRK1001 is a controller specially designed for synchronous rectification in flyback converters operating in QR or mixed CCM/DCM fixed frequency. In this application the SRK1001 is configured for QR operation.

This controller turns on the synchronous rectification Power MOSFET Q2 during the demagnetization period and the energy stored in the transformer primary inductance is transferred to the secondary side.

The current flows through SR Power MOSFET Q2 to the output capacitors C9 and C10, until the transformer is completely demagnetized. These capacitors ensure an ESR that is as low as possible and sufficient AC ripple capability. Capacitor C27 further reduces the output switching noise.

For a further understanding of SRK1001 operation, please refer to its datasheet (2).

The synchronous rectification Power MOSFET Q2 is a PowerFLAT N-channel 100 V Power MOSFET that utilizes STripFET F7 technology with  $R_{DS(ON)} = 0.006 \Omega$ . This technology features an enhanced trench-gate structure that lowers device on-state resistance, while also reducing internal capacitances and gate charge for faster and more efficient switching.

## 6.6 USB Power Delivery controller

STUSB4761 offers the benefits of a full hardware USB PD stack allowing robust, deterministic and safe negotiation in line with USB PD standards. It is ideal for provider application in which digital or software intelligence is limited or missing.

STUSB4761 main functions are to:

1. Detect the connection between two ports (attach detection),
2. Establish a valid Source-to-Sink connection,
3. Determine the attached device mode: Sink or Accessory,
4. Check cable power capabilities,
5. Negotiate a USB PD contract with a PD capable device,
6. Configure the output power path accordingly,
7. Regulate Voltage and Current according to PD contract,
8. Monitor VBUS, manage transitions, handle protections and ensure user and device safety

Additionally, the STUSB4761 offers customizable Power Data Objects (PDO) and UVLO / OVLO protections, an integrated discharge path, a VBUS current mirror and is natively robust to High Voltage surge, including on the CC pins.

In the EVLSTCH03-45WPD evaluation board, the STUSB4761 is used with its default factory setting except for Voltage UVLO for SRC\_PDO1 set to -10%, summarized in the table below:

**Table 4. STUSB4761 configuration**

| PDO #    | PD Power<br>(default) <sup>(1)</sup> | PD Power<br>(OTP) <sup>(1)</sup> | Voltage<br>UVLO <sup>(2)</sup> | Voltage<br>OVLO <sup>(2)</sup> |
|----------|--------------------------------------|----------------------------------|--------------------------------|--------------------------------|
| SRC_PDO1 | 5 V - 3 A                            | 2 A                              | -10%                           | +10%                           |
| SRC_PDO2 | 9 V - 3 A                            | 2 A                              | -5%                            | +10%                           |
| SRC_PDO3 | 12 V - 3 A                           | 2 A                              | -5%                            | +10%                           |
| SRC_PDO4 | 15 V - 3 A                           | 2 A                              | -5%                            | +10%                           |
| SRC_PDO5 | 20 V - 2.25 A                        | 2 A                              | -5%                            | +10%                           |

1. PD Power (PDP): The output power of a Source, as specified by the manufacturer and expressed in Fixed Supply PDOs.


2. UVLO / OVLO accuracy: +/- 2% across temperature range

The on-board temperature is monitored: in case of over-temperature conditions, (by default 70°C) the STUSB4761 advertises lower power profiles.

VBUS current used for regulation is measured thanks to a 10 mΩ (default) shunt resistor between VDD and ISENSE\_DISCH pins. In case the measured VBUS current reaches the regulation threshold (+12.5% above the SRC current from the PDO selected by the sink), the STUSB4761 enters in CC mode: voltage is decreased down to the undervoltage (UVLO) condition defined for the selected contract.

To guarantee the regulation accuracy, one must follow the shunt layout recommendations as shown in [Figure 14](#) below. A more detailed description of how to route the STUSB4761 PCB can be found in the AN5430 Application Note (3).

Figure 14. STUSB4761 layout recommendations

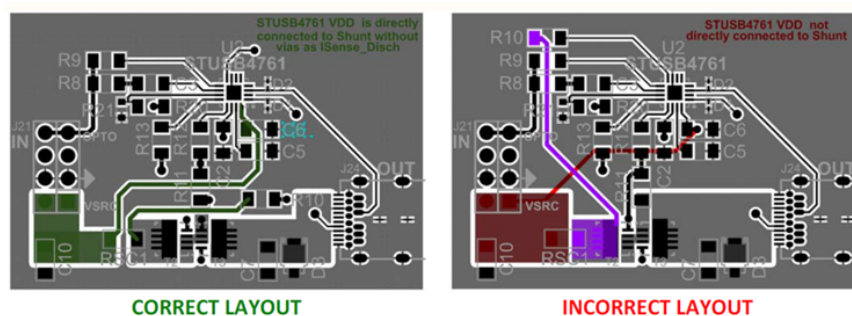

STUSB4761 NVM configuration can be customized statically to align PD controller behavior according to final application requirements. Customization applies to various parameters such as number of PDO, voltage, current, discharge time, protection thresholds, etc...

Parameter customization is possible:

- Either by direct access through I<sup>2</sup>C interface,
- Or by using specific commands packaged as ST proprietary unstructured VDM when STUSB4761 is connected in debug accessory mode (OrientedDebug Accessory.SRC state)

A more detailed description of temperature adaptive power, factory settings and customization can be found in the STUSB4761 datasheet or product page (4).


## 7 Typical waveforms

In this section the converter operating waveforms are shown, in particular the waveforms of the primary and secondary are reported in various line and load conditions.

### 7.1 Start-up waveforms


The following figures show the startup of the converter at 115 V<sub>AC</sub> and 230 V<sub>AC</sub> under no load and full load conditions. The output voltage begins to increase after a short delay from the presence of the input voltage (< 300 ms). No abnormal oscillation in the output is present.

**Figure 15. Start-up waveforms at 115 V<sub>AC</sub> - No load**

 


Violet = V<sub>IN</sub> 200 V/div, Blue = V<sub>OUT</sub> 2.5 V/div,  
Green = I<sub>OUT</sub> 1.5 A/div

**Figure 16. Start-up waveforms at 115 V<sub>AC</sub> - Full load**

 


Violet = V<sub>IN</sub> 200 V/div, Blue = V<sub>OUT</sub> 2.5 V/div,  
Green = I<sub>OUT</sub> 1.5 A/div

**Figure 17. Start-up waveforms at 230 V<sub>AC</sub> - No load**

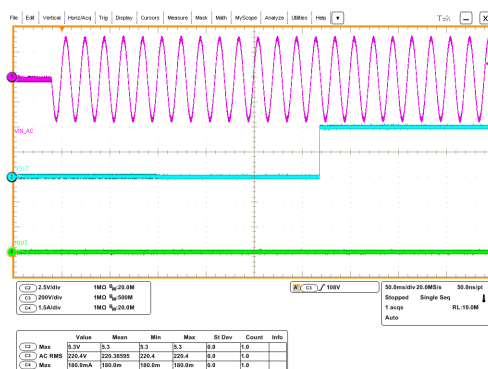

Violet = V<sub>IN</sub> 200 V/div, Blue = V<sub>OUT</sub> 2.5 V/div,  
Green = I<sub>OUT</sub> 1.5 A/div

**Figure 18. Start-up waveforms at 230 V<sub>AC</sub> Full load**

 


Violet = V<sub>IN</sub> 200 V/div, Blue = V<sub>OUT</sub> 2.5 V/div,  
Green = I<sub>OUT</sub> 1.5 A/div

## 7.2 Primary drain voltage and current sense voltage


The following figures shows the drain voltage and the current sense pin voltage waveforms of the flyback converter at 90 V<sub>AC</sub> and 265 V<sub>AC</sub> under full load condition.

**Figure 19. Flyback primary side waveforms at V<sub>OUT</sub> = 5 V - I<sub>OUT</sub> = 3 A (V<sub>IN</sub> = 90 V<sub>AC</sub>)**

 

Blue = V<sub>DS</sub> 70 V/div, Green = V<sub>SENSE</sub> 300 mV/div ;  
V<sub>DS-MAX</sub> = 249.2 V

**Figure 20. Flyback primary side waveforms at V<sub>OUT</sub> = 5 V - I<sub>OUT</sub> = 3 A (V<sub>IN</sub> = 265 V<sub>AC</sub>)**

 


Blue = V<sub>DS</sub> 100 V/div, Green = V<sub>SENSE</sub> 300 mV/div ;  
V<sub>DS-MAX</sub> = 492 V

**Figure 21. Flyback primary side waveforms at V<sub>OUT</sub> = 9 V - I<sub>OUT</sub> = 3 A (V<sub>IN</sub> = 90 V<sub>AC</sub>)**



Blue = V<sub>DS</sub> 70 V/div, Green = V<sub>SENSE</sub> 300 mV/div ;  
V<sub>DS-MAX</sub> = 294 V


**Figure 22. Flyback primary side waveforms at V<sub>OUT</sub> = 9 V - I<sub>OUT</sub> = 3 A (V<sub>IN</sub> = 265 V<sub>AC</sub>)**

 

 Blue = V<sub>DS</sub> 100 V/div, Green = V<sub>SENSE</sub> 300 mV/div ;  
V<sub>DS-MAX</sub> = 532 V

 


**Figure 23. Flyback primary side waveforms at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**




Blue =  $V_{DS}$  70 V/div, Green =  $V_{SENSE}$  300 mV/div ;  
 $V_{DS-MAX} = 327.6\text{ V}$

**Figure 24. Flyback primary side waveforms at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**




Blue =  $V_{DS}$  100 V/div, Green =  $V_{SENSE}$  300 mV/div ;  
 $V_{DS-MAX} = 564\text{ V}$

**Figure 25. Flyback primary side waveforms at  $V_{OUT} = 15\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  70 V/div, Green =  $V_{SENSE}$  300 mV/div ;  
 $V_{DS-MAX} = 361.2\text{ V}$

**Figure 26. Flyback primary side waveforms at  $V_{OUT} = 15\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  100 V/div, Green =  $V_{SENSE}$  300 mV/div ;  
 $V_{DS-MAX} = 588\text{ V}$

**Figure 27. Flyback primary side waveforms at  $V_{OUT} = 20\text{ V}$  -  $I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**

 

Blue =  $V_{DS}$  70 V/div, Green =  $V_{SENSE}$  300 mV/div ;  
 $V_{DS-MAX} = 378\text{ V}$

**Figure 28. Flyback primary side waveforms at  $V_{OUT} = 20\text{ V}$  -  $I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  100 V/div, Green =  $V_{SENSE}$  300 mV/div ;  
 $V_{DS-MAX} = 628\text{ V}$

## 7.3 Secondary drain voltage and current


The following figures show the drain voltage and the drain current waveforms of operation of the flyback converter at 90  $V_{AC}$  and 265  $V_{AC}$  under full load condition.

**Figure 29. Flyback secondary side waveforms at  $V_{OUT} = 5\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  20 V/div, Green =  $I_{DS}$  10 A/div ;  
 $V_{DS-MAX} = 29.6\text{ V}$

**Figure 30. Flyback secondary side waveforms at  $V_{OUT} = 5\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  100 V/div, Green =  $I_{DS}$  10 A/div ;  
 $V_{DS-MAX} = 88\text{ V}$

**Figure 31. Flyback secondary side waveforms at  $V_{OUT} = 9\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  20 V/div, Green =  $I_{DS}$  10 A/div ;  
 $V_{DS-MAX} = 31.2\text{ V}$

**Figure 32. Flyback secondary side waveforms at  $V_{OUT} = 9\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  100 V/div, Green =  $I_{DS}$  10 A/div ;  
 $V_{DS-MAX} = 88\text{ V}$

**Figure 33. Flyback secondary side waveforms at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  20 V/div, Green =  $I_{DS}$  10 A/div ;  
 $V_{DS-MAX} = 33.6\text{ V}$

**Figure 34. Flyback secondary side waveforms at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**

 

Blue =  $V_{DS}$  100 V/div, Green =  $I_{DS}$  10 A/div ;  
 $V_{DS-MAX} = 87.2\text{ V}$


**Figure 35. Flyback secondary side waveforms at  $V_{OUT} = 15\text{ V} - I_{OUT} = 3\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**

 

Blue =  $V_{DS}$  20 V/div, Green =  $I_{DS}$  10 A/div ;

$V_{DS-MAX} = 36.8\text{ V}$


**Figure 36. Flyback secondary side waveforms at  $V_{OUT} = 15\text{ V} - I_{OUT} = 3\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**

 

Blue =  $V_{DS}$  100 V/div, Green =  $I_{DS}$  10 A/div ;

$V_{DS-MAX} = 88.8\text{ V}$


**Figure 37. Flyback secondary side waveforms at  $V_{OUT} = 20\text{ V} - I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 90\text{ V}_{AC}$ )**

 

Blue =  $V_{DS}$  20 V/div, Green =  $I_{DS}$  10 A/div ;

$V_{DS-MAX} = 40\text{ V}$

**Figure 38. Flyback secondary side waveforms at  $V_{OUT} = 20\text{ V} - I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 265\text{ V}_{AC}$ )**

 


Blue =  $V_{DS}$  100 V/div, Green =  $I_{DS}$  10 A/div ;

$V_{DS-MAX} = 89.6\text{ V}$


## 7.4 Load transient response

The following figures show the load transient response waveforms of the flyback converter subjected to repetitive dynamic load transitions zero to full load at 115  $V_{AC}$  and 230  $V_{AC}$ . They show no abnormal oscillation in the output and the overshoot and undershoot values are acceptable.

 **Figure 39. Dynamic load transient zero to full load at  $V_{OUT} = 5\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**

 
 
Blue =  $V_{OUT}$  1 V/div, Green =  $I_{OUT}$  1 A/div

$V_{OUT-MAX} = 5.32\text{ V}$  ;  $V_{OUT-MIN} = 4.7\text{ V}$

**Figure 40. Dynamic load transient zero to full load at  $V_{OUT} = 5\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**


 
Blue =  $V_{OUT}$  1 V/div, Green =  $I_{OUT}$  1 A/div

$V_{OUT-MAX} = 5.32\text{ V}$  ;  $V_{OUT-MIN} = 4.7\text{ V}$

**Figure 41. Dynamic load transient zero to full load at  $V_{OUT} = 9\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**


Blue =  $V_{OUT}$  1 V/div, Green =  $I_{OUT}$  1 A/div

$V_{OUT-MAX} = 9.48\text{ V}$  ;  $V_{OUT-MIN} = 8.84\text{ V}$

**Figure 42. Dynamic load transient zero to full load at  $V_{OUT} = 9\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**


Blue =  $V_{OUT}$  1 V/div, Green =  $I_{OUT}$  1 A/div

$V_{OUT-MAX} = 9.44\text{ V}$  ;  $V_{OUT-MIN} = 8.84\text{ V}$

**Figure 43. Dynamic load transient zero to full load at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**


Blue =  $V_{OUT}$  1.4 V/div, Green =  $I_{OUT}$  1 A/div

$V_{OUT-MAX} = 12.6\text{ V}$  ;  $V_{OUT-MIN} = 11.87\text{ V}$

**Figure 44. Dynamic load transient zero to full load at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**


Blue =  $V_{OUT}$  1.4 V/div, Green =  $I_{OUT}$  1 A/div

 
$V_{OUT-MAX} = 12.54\text{ V}$  ;  $V_{OUT-MIN} = 11.87\text{ V}$

**Figure 45. Dynamic load transient zero to full load at  $V_{OUT} = 15\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**

 

Blue =  $V_{OUT}$  1.7 V/div, Green =  $I_{OUT}$  1 A/div  
 $V_{OUT-MAX} = 15.71\text{ V}$  ;  $V_{OUT-MIN} = 14.89\text{ V}$

**Figure 46. Dynamic load transient zero to full load at  $V_{OUT} = 15\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**


Blue =  $V_{OUT}$  1.7 V/div, Green =  $I_{OUT}$  1 A/div  
 $V_{OUT-MAX} = 15.71\text{ V}$  ;  $V_{OUT-MIN} = 14.89\text{ V}$

**Figure 47. Dynamic load transient zero to full load at  $V_{OUT} = 20\text{ V}$  -  $I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**


 
 
 
 
 
 
Blue =  $V_{OUT}$  2.2 V/div, Green =  $I_{OUT}$  1 A/div  
 $V_{OUT-MAX} = 20.86\text{ V}$  ;  $V_{OUT-MIN} = 19.89\text{ V}$

**Figure 48. Dynamic load transient zero to full load at  $V_{OUT} = 20\text{ V}$  -  $I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**


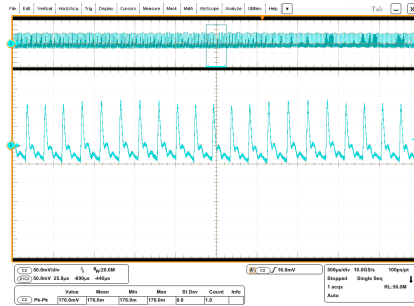
Blue =  $V_{OUT}$  2.2 V/div, Green =  $I_{OUT}$  1 A/div  
 $V_{OUT-MAX} = 20.86\text{ V}$  ;  $V_{OUT-MIN} = 20.86\text{ V}$

## 7.5 Output voltage ripple

The following figures show the output voltage ripple waveforms of the flyback converter at 115  $V_{AC}$  and 230  $V_{AC}$  under full load condition.


**Figure 49. Output voltage ripple at  $V_{OUT} = 5\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**

Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 104\text{ mV}$ 
**Figure 50. Output voltage ripple at  $V_{OUT} = 5\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**

Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 98\text{ mV}$ 
**Figure 51. Output voltage ripple at  $V_{OUT} = 9\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**

Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 130\text{ mV}$ 
**Figure 52. Output voltage ripple at  $V_{OUT} = 9\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**

Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 128\text{ mV}$ 
**Figure 53. Output voltage ripple at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**

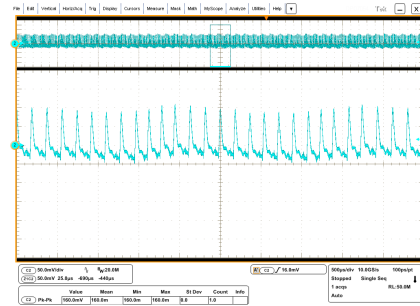Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 150\text{ mV}$ 
**Figure 54. Output voltage ripple at  $V_{OUT} = 12\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**

Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 144\text{ mV}$

**Figure 55. Output voltage ripple at  $V_{OUT} = 15\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**




Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 176\text{ mV}$

**Figure 56. Output voltage ripple at  $V_{OUT} = 15\text{ V}$  -  $I_{OUT} = 3\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**




Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 160\text{ mV}$

**Figure 57. Output voltage ripple at  $V_{OUT} = 20\text{ V}$  -  $I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 115\text{ V}_{AC}$ )**

 

Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 176\text{ mV}$

**Figure 58. Output voltage ripple at  $V_{OUT} = 20\text{ V}$  -  $I_{OUT} = 2.25\text{ A}$  ( $V_{IN} = 230\text{ V}_{AC}$ )**

 

Blue =  $V_{OUT}$  50 mV/div AC ;  $V_{OUT-PKPK} = 178\text{ mV}$



## 8 Efficiency and no-load consumption measurements

The energy efficiency of the adapter meets all DOE and UE CoC requirements, since the 4 points average efficiency and efficiency at 10% of rated load are always higher than the most stringent EU CoC rev. 5 - Tier 2 (2016).

The adapter efficiency and no-load consumption are measured at nominal input voltages and in the various operating profiles.

### 8.1 Efficiency performance at 115 V<sub>AC</sub>

**Table 5.** Efficiency measurements summary at V<sub>IN</sub> = 115 V<sub>AC</sub> / 60 Hz

| Efficiency @ V <sub>IN</sub> = 115 V <sub>AC</sub> / 60 Hz |                |       |       |       |       |
|--|----------------|-------|-------|-------|-------|
| % of rated power   | Output profile |       |       |       |       |
|  | 5V             | 9V    | 12V   | 15V   | 20V   |
| 25%  | 87.92          | 90.18 | 90.32 | 90.22 | 89.48 |
| 50%  | 88.38          | 90.80 | 90.97 | 90.99 | 90.72 |
| 75%  | 87.97          | 90.65 | 90.92 | 91.03 | 90.91 |
| 100%   | 87.39          | 90.35 | 90.70 | 90.81 | 90.61 |
| Avg eff. %   | 87.92          | 90.50 | 90.73 | 90.76 | 90.43 |
| EU CoC rev. 5 - Tier 2 limit                               | 81.84          | 87.30 | 88.30 | 88.85 | 88.85 |
| 10%  | 85.36          | 86.97 | 86.99 | 87.33 | 85.53 |
| EU CoC rev. 5 - Tier 2 limit                               | 72.48          | 77.30 | 78.30 | 78.85 | 78.85 |


### 8.2 Efficiency performance at 230 V<sub>AC</sub>

**Table 6.** Efficiency measurements summary at V<sub>IN</sub> = 230 V<sub>AC</sub> / 50 Hz

| Efficiency @ V <sub>IN</sub> = 230 V <sub>AC</sub> / 60 Hz |                |       |       |       |       |
|--|----------------|-------|-------|-------|-------|
| % of rated power   | Output profile |       |       |       |       |
|  | 5V             | 9V    | 12V   | 15V   | 20V   |
| 25%  | 82.00          | 87.07 | 88.06 | 88.66 | 87.88 |
| 50%  | 85.84          | 89.48 | 90.23 | 90.14 | 90.27 |
| 75%  | 86.59          | 90.15 | 90.89 | 91.31 | 91.14 |
| 100%   | 86.70          | 90.39 | 91.16 | 91.62 | 91.58 |
| Avg eff. %   | 85.29          | 89.27 | 90.09 | 90.43 | 90.22 |
| EU CoC rev. 5 - Tier 2 limit                               | 81.84          | 87.30 | 88.30 | 88.85 | 88.85 |
| 10%  | 74.90          | 78.71 | 80.65 | 82.01 | 80.74 |
| EU CoC rev. 5 - Tier 2 limit                               | 72.48          | 77.30 | 78.30 | 78.85 | 78.85 |


### 8.3 Output profile 5 V / 3 A

Figure 59. Efficiency vs. output power at  $V_{OUT} = 5\text{ V}$

 


### 8.4 Output profile 9 V / 3 A

Figure 60. Efficiency vs. output power at  $V_{OUT} = 9\text{ V}$

 


### 8.5 Output profile 12 V / 3 A

Figure 61. Efficiency vs. output power at  $V_{OUT} = 12\text{ V}$

 


## 8.6 Output profile 15 V / 3 A

Figure 62. Efficiency vs. output power at  $V_{OUT} = 15\text{ V}$

 

## 8.7 Output profile 20 V / 2.25 A

Figure 63. Efficiency vs. output power at  $V_{OUT} = 20\text{ V}$

 

## 8.8 No-load consumption performance

The no-load consumption is measured at nominal input voltage with the USB Type-C interface board for output voltage selection disconnected from the adapter. In this way, the output voltage profile is set by default to 5 V / 3 A.


Table 7. No-Load consumption measurements

| Input voltage $V_{IN}$ | No-load consumption [mW] |
|------------------------|--------------------------|
| 115 $V_{AC}$ / 60 Hz   | 14.71                    |
| 230 $V_{AC}$ / 50 Hz   | 18.42                    |

## 9 Thermal measurements


A thermal analysis of the board was performed with an infrared thermal imaging camera. The test was conducted with the output voltage profile selected to 15 V and full load. The board was submitted at minimum voltage and maximum voltage and after 30 minutes while the input voltage minimum and maximum input voltage 90 V<sub>AC</sub> and 265 V<sub>AC</sub> respectively.

**Figure 64. Thermal image at 90 V<sub>AC</sub> (top side)**

 


V<sub>OUT</sub> = 15 V ; I<sub>OUT</sub> = 3 A

**Figure 65. Thermal image at 90 V<sub>AC</sub> (bottom side)**

 


V<sub>OUT</sub> = 15 V ; I<sub>OUT</sub> = 3 A

**Figure 66. Thermal image at 265 V<sub>AC</sub> (top side)**

 

V<sub>OUT</sub> = 15 V ; I<sub>OUT</sub> = 3 A

**Figure 67. Thermal image at 265 V<sub>AC</sub> (bottom side)**

 

V<sub>OUT</sub> = 15 V ; I<sub>OUT</sub> = 3 A

## 10 Conducted EMI

A pre-compliance test for EN55022 – Class B European regulation for domestic equipment is performed, measuring the line conducted noise emissions at nominal mains voltages and full load.


The various measurements shown below have been performed using the average EMI detector configuration of the EMC analyzer receiver.

The Class B limits for domestic equipment are more severe compared to the Class A requirements, dedicated to information technology equipment. The lower limit in the graphs refers to the Class B average measurement set-up.


The results show a comfortable margin between the measurements and the required limits.

### 10.1 Output profile: 5 V / 3 A


**Figure 68. EMI measurements for 5 V output profile, Line scan (115 V<sub>AC</sub>)**

 


**Figure 69. EMI measurements for 5 V output profile, Line scan (230 V<sub>AC</sub>)**

 

**Figure 70. EMI measurements for 5 V output profile, Neutral scan (115 V<sub>AC</sub>)**

 


**Figure 71. EMI measurements for 5 V output profile, Neutral scan (230 V<sub>AC</sub>)**

 


## 10.2 Output profile: 9 V / 3 A


**Figure 72. EMI measurements for 9 V output profile, Line scan (115 V<sub>AC</sub>)**

 


**Figure 73. EMI measurements for 9 V output profile, Line scan (230 V<sub>AC</sub>)**

 

**Figure 74. EMI measurements for 9 V output profile, Neutral scan (115 V<sub>AC</sub>)**

 


**Figure 75. EMI measurements for 9 V output profile, Neutral scan (230 V<sub>AC</sub>)**

  




## 10.3 Output profile: 12 V / 3 A

**Figure 76. EMI measurements for 12 V output profile, Line scan (115 V<sub>AC</sub>)**







**Figure 77. EMI measurements for 12 V output profile, Line scan (230 V<sub>AC</sub>)**

       

**Figure 78. EMI measurements for 12 V output profile, Neutral scan (115 V<sub>AC</sub>)**

**Figure 79. EMI measurements for 12 V output profile, Neutral scan (230 V<sub>AC</sub>)**


 
## 10.4

### Output profile: 15 V / 3 A

 
**Figure 80. EMI measurements for 15 V output profile, Line scan (115 V<sub>AC</sub>)**

**Figure 81. EMI measurements for 15 V output profile, Line scan (230 V<sub>AC</sub>)**

**Figure 82. EMI measurements for 15 V output profile, Neutral scan (115 V<sub>AC</sub>)**

**Figure 83. EMI measurements for 15 V output profile, Neutral scan (230 V<sub>AC</sub>)**


## 10.5 Output profile: 20 V / 2.25 A


**Figure 84. EMI measurements for 20 V output profile, Line scan (115 V<sub>AC</sub>)**




**Figure 85. EMI measurements for 20 V output profile, Line scan (230 V<sub>AC</sub>)**



**Figure 86. EMI measurements for 20 V output profile, Neutral scan (115 V<sub>AC</sub>)**

 

**Figure 87. EMI measurements for 20 V output profile, Neutral scan (230 V<sub>AC</sub>)**

 



## **11**      **Reference**

---

- (1) STCH03 Datasheet: available at [www.st.com](http://www.st.com)
- (2) SRK1001 Datasheet: available at [www.st.com](http://www.st.com)
- (3) AN5430 " The STUSB4761 PCB routing guidelines" : available at [www.st.com](http://www.st.com)
- (4) STUSB4761 Datasheet: available at [www.st.com](http://www.st.com)

## Revision history

**Table 8. Document revision history**

| Date        | Version | Changes          |
|-------------|---------|------------------|
| 19-Feb-2020 | 1       | Initial release. |

## Contents

|          |   |           |
|----------|---|-----------|
| <b>1</b> | <b>Introduction chapter 1</b>                               | <b>2</b>  |
| <b>2</b> | <b>Specifications</b>                                       | <b>3</b>  |
| <b>3</b> | <b>Schematic</b>  | <b>4</b>  |
| <b>4</b> | <b>Bill of materials</b>                                    | <b>5</b>  |
| <b>5</b> | <b>PCB layout</b>   | <b>8</b>  |
| <b>6</b> | <b>Board description</b>                                    | <b>9</b>  |
| 6.1      | Input stage and filtering                                   | 9         |
| 6.2      | Flyback controller and primary MOSFET                       | 9         |
| 6.2.1    | Power MOSFET selection                                      | 10        |
| 6.2.2    | Turns ratio transformer selection                           | 11        |
| 6.2.3    | Current sense resistor selection                            | 11        |
| 6.2.4    | Zero current resistor selection                             | 12        |
| 6.2.5    | UVP – OVP resistor selection                                | 13        |
| 6.3      | Snubber circuit   | 15        |
| 6.4      | Transformer specification                                   | 15        |
| 6.5      | Synchronous rectifier controller and secondary Power MOSFET | 16        |
| 6.6      | USB Power Delivery controller                               | 16        |
| <b>7</b> | <b>Typical waveforms</b>                                    | <b>19</b> |
| 7.1      | Start-up waveforms  | 19        |
| 7.2      | Primary drain voltage and current sense voltage             | 19        |
| 7.3      | Secondary drain voltage and current                         | 22        |
| 7.4      | Load transient response                                     | 24        |
| 7.5      | Output voltage ripple                                       | 26        |
| <b>8</b> | <b>Efficiency and no-load consumption measurements</b>      | <b>29</b> |
| 8.1      | Efficiency performance at 115 V <sub>AC</sub>               | 29        |
| 8.2      | Efficiency performance at 230 V <sub>AC</sub>               | 29        |
| 8.3      | Output profile 5 V / 3 A                                    | 29        |
| 8.4      | Output profile 9 V / 3 A                                    | 30        |
| 8.5      | Output profile 12 V / 3 A                                   | 30        |

|           |                                       |           |
|-----------|---------------------------------------|-----------|
| 8.6       | Output profile 15 V / 3 A .....       | 30        |
| 8.7       | Output profile 20 V / 2.25 A .....    | 31        |
| 8.8       | No-load consumption performance ..... | 31        |
| <b>9</b>  | <b>Thermal measurements .....</b>     | <b>32</b> |
| <b>10</b> | <b>Conducted EMI .....</b>            | <b>33</b> |
| 10.1      | Output profile: 5 V / 3 A .....       | 33        |
| 10.2      | Output profile: 9 V / 3 A .....       | 33        |
| 10.3      | Output profile: 12 V / 3 A .....      | 34        |
| 10.4      | Output profile: 15 V / 3 A .....      | 35        |
| 10.5      | Output profile: 20 V / 2.25 A .....   | 35        |
| <b>11</b> | <b>Reference .....</b>                | <b>37</b> |
|           | <b>Revision history .....</b>         | <b>38</b> |
|           | <b>Contents .....</b>                 | <b>39</b> |
|           | <b>List of tables .....</b>           | <b>41</b> |
|           | <b>List of figures .....</b>          | <b>42</b> |

## List of tables

|                 |  |    |
|-----------------|--|----|
| <b>Table 1.</b> | EVLSTCH03-45WPD evaluation board specifications . . . . .                          | 3  |
| <b>Table 2.</b> | EVLSTCH03-45WPD evaluation board bill of materials . . . . .                       | 5  |
| <b>Table 3.</b> | Transformer electrical specifications . . . . .                                    | 16 |
| <b>Table 4.</b> | STUSB4761 configuration . . . . .  | 17 |
| <b>Table 5.</b> | Efficiency measurements summary at $V_{IN} = 115 V_{AC} / 60 \text{ Hz}$ . . . . . | 29 |
| <b>Table 6.</b> | Efficiency measurements summary at $V_{IN} = 230 V_{AC} / 50 \text{ Hz}$ . . . . . | 29 |
| <b>Table 7.</b> | No-Load consumption measurements . . . . .   | 31 |
| <b>Table 8.</b> | Document revision history . . . . .  | 38 |

## List of figures

|            |  |    |
|------------|--|----|
| Figure 1.  | EVLSTCH03-45WPD evaluation board   | 1  |
| Figure 2.  | EVLSTCH03-45WPD evaluation board block diagram   | 2  |
| Figure 3.  | EVLSTCH03-45WPD evaluation board schematic   | 4  |
| Figure 4.  | EVLSTCH03-45WPD PCB top layer layout   | 8  |
| Figure 5.  | EVLSTCH03-45WPD PCB bottom layer layout  | 8  |
| Figure 6.  | EVLSTCH03-45WPD top view   | 9  |
| Figure 7.  | EVLSTCH03-45WPD bottom view  | 9  |
| Figure 8.  | STCH03 configuration basic   | 10 |
| Figure 9.  | Voltage between drain and source of the Power MOSFET, $V_{DS}$   | 11 |
| Figure 10. | Splitting of the $R_{ZCD}$ resistor  | 13 |
| Figure 11. | ZCD operational phases   | 13 |
| Figure 12. | Splitting of the OVP and UVP threshold   | 15 |
| Figure 13. | Transformer electrical diagram   | 16 |
| Figure 14. | STUSB4761 layout recommendations   | 18 |
| Figure 15. | Start-up waveforms at 115 V <sub>AC</sub> - No load  | 19 |
| Figure 16. | Start-up waveforms at 115 V <sub>AC</sub> - Full load  | 19 |
| Figure 17. | Start-up waveforms at 230 V <sub>AC</sub> - No load  | 19 |
| Figure 18. | Start-up waveforms at 230 V <sub>AC</sub> Full load  | 19 |
| Figure 19. | Flyback primary side waveforms at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )                | 20 |
| Figure 20. | Flyback primary side waveforms at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )               | 20 |
| Figure 21. | Flyback primary side waveforms at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )                | 20 |
| Figure 22. | Flyback primary side waveforms at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )               | 20 |
| Figure 23. | Flyback primary side waveforms at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )               | 21 |
| Figure 24. | Flyback primary side waveforms at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )              | 21 |
| Figure 25. | Flyback primary side waveforms at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )               | 21 |
| Figure 26. | Flyback primary side waveforms at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )              | 21 |
| Figure 27. | Flyback primary side waveforms at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )            | 22 |
| Figure 28. | Flyback primary side waveforms at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )           | 22 |
| Figure 29. | Flyback secondary side waveforms at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )              | 22 |
| Figure 30. | Flyback secondary side waveforms at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )             | 22 |
| Figure 31. | Flyback secondary side waveforms at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )              | 23 |
| Figure 32. | Flyback secondary side waveforms at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )             | 23 |
| Figure 33. | Flyback secondary side waveforms at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )             | 23 |
| Figure 34. | Flyback secondary side waveforms at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )            | 23 |
| Figure 35. | Flyback secondary side waveforms at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )             | 24 |
| Figure 36. | Flyback secondary side waveforms at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )            | 24 |
| Figure 37. | Flyback secondary side waveforms at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 90\text{ V}_{AC}$ )          | 24 |
| Figure 38. | Flyback secondary side waveforms at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 265\text{ V}_{AC}$ )         | 24 |
| Figure 39. | Dynamic load transient zero to full load at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ )     | 25 |
| Figure 40. | Dynamic load transient zero to full load at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ )     | 25 |
| Figure 41. | Dynamic load transient zero to full load at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ )     | 25 |
| Figure 42. | Dynamic load transient zero to full load at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ )     | 25 |
| Figure 43. | Dynamic load transient zero to full load at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ )    | 25 |
| Figure 44. | Dynamic load transient zero to full load at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ )    | 25 |
| Figure 45. | Dynamic load transient zero to full load at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ )    | 26 |
| Figure 46. | Dynamic load transient zero to full load at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ )    | 26 |
| Figure 47. | Dynamic load transient zero to full load at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ ) | 26 |
| Figure 48. | Dynamic load transient zero to full load at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ ) | 26 |

|                   |   |    |
|-------------------|---|----|
| <b>Figure 49.</b> | Output voltage ripple at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ ) . . . . .     | 27 |
| <b>Figure 50.</b> | Output voltage ripple at $V_{OUT} = 5\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ ) . . . . .     | 27 |
| <b>Figure 51.</b> | Output voltage ripple at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ ) . . . . .     | 27 |
| <b>Figure 52.</b> | Output voltage ripple at $V_{OUT} = 9\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ ) . . . . .     | 27 |
| <b>Figure 53.</b> | Output voltage ripple at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ ) . . . . .    | 27 |
| <b>Figure 54.</b> | Output voltage ripple at $V_{OUT} = 12\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ ) . . . . .    | 27 |
| <b>Figure 55.</b> | Output voltage ripple at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ ) . . . . .    | 28 |
| <b>Figure 56.</b> | Output voltage ripple at $V_{OUT} = 15\text{ V}$ - $I_{OUT} = 3\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ ) . . . . .    | 28 |
| <b>Figure 57.</b> | Output voltage ripple at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 115\text{ V}_{AC}$ ) . . . . . | 28 |
| <b>Figure 58.</b> | Output voltage ripple at $V_{OUT} = 20\text{ V}$ - $I_{OUT} = 2.25\text{ A}$ ( $V_{IN} = 230\text{ V}_{AC}$ ) . . . . . | 28 |
| <b>Figure 59.</b> | Efficiency vs. output power at $V_{OUT} = 5\text{ V}$ . . . . .   | 30 |
| <b>Figure 60.</b> | Efficiency vs. output power at $V_{OUT} = 9\text{ V}$ . . . . .   | 30 |
| <b>Figure 61.</b> | Efficiency vs. output power at $V_{OUT} = 12\text{ V}$ . . . . .  | 30 |
| <b>Figure 62.</b> | Efficiency vs. output power at $V_{OUT} = 15\text{ V}$ . . . . .  | 31 |
| <b>Figure 63.</b> | Efficiency vs. output power at $V_{OUT} = 20\text{ V}$ . . . . .  | 31 |
| <b>Figure 64.</b> | Thermal image at $90\text{ V}_{AC}$ (top side) . . . . .  | 32 |
| <b>Figure 65.</b> | Thermal image at $90\text{ V}_{AC}$ (bottom side) . . . . .   | 32 |
| <b>Figure 66.</b> | Thermal image at $265\text{ V}_{AC}$ (top side) . . . . .   | 32 |
| <b>Figure 67.</b> | Thermal image at $265\text{ V}_{AC}$ (bottom side) . . . . .  | 32 |
| <b>Figure 68.</b> | EMI measurements for $5\text{ V}$ output profile, Line scan ( $115\text{ V}_{AC}$ ) . . . . .                           | 33 |
| <b>Figure 69.</b> | EMI measurements for $5\text{ V}$ output profile, Line scan ( $230\text{ V}_{AC}$ ) . . . . .                           | 33 |
| <b>Figure 70.</b> | EMI measurements for $5\text{ V}$ output profile, Neutral scan ( $115\text{ V}_{AC}$ ) . . . . .                        | 33 |
| <b>Figure 71.</b> | EMI measurements for $5\text{ V}$ output profile, Neutral scan ( $230\text{ V}_{AC}$ ) . . . . .                        | 33 |
| <b>Figure 72.</b> | EMI measurements for $9\text{ V}$ output profile, Line scan ( $115\text{ V}_{AC}$ ) . . . . .                           | 34 |
| <b>Figure 73.</b> | EMI measurements for $9\text{ V}$ output profile, Line scan ( $230\text{ V}_{AC}$ ) . . . . .                           | 34 |
| <b>Figure 74.</b> | EMI measurements for $9\text{ V}$ output profile, Neutral scan ( $115\text{ V}_{AC}$ ) . . . . .                        | 34 |
| <b>Figure 75.</b> | EMI measurements for $9\text{ V}$ output profile, Neutral scan ( $230\text{ V}_{AC}$ ) . . . . .                        | 34 |
| <b>Figure 76.</b> | EMI measurements for $12\text{ V}$ output profile, Line scan ( $115\text{ V}_{AC}$ ) . . . . .                          | 34 |
| <b>Figure 77.</b> | EMI measurements for $12\text{ V}$ output profile, Line scan ( $230\text{ V}_{AC}$ ) . . . . .                          | 34 |
| <b>Figure 78.</b> | EMI measurements for $12\text{ V}$ output profile, Neutral scan ( $115\text{ V}_{AC}$ ) . . . . .                       | 35 |
| <b>Figure 79.</b> | EMI measurements for $12\text{ V}$ output profile, Neutral scan ( $230\text{ V}_{AC}$ ) . . . . .                       | 35 |
| <b>Figure 80.</b> | EMI measurements for $15\text{ V}$ output profile, Line scan ( $115\text{ V}_{AC}$ ) . . . . .                          | 35 |
| <b>Figure 81.</b> | EMI measurements for $15\text{ V}$ output profile, Line scan ( $230\text{ V}_{AC}$ ) . . . . .                          | 35 |
| <b>Figure 82.</b> | EMI measurements for $15\text{ V}$ output profile, Neutral scan ( $115\text{ V}_{AC}$ ) . . . . .                       | 35 |
| <b>Figure 83.</b> | EMI measurements for $15\text{ V}$ output profile, Neutral scan ( $230\text{ V}_{AC}$ ) . . . . .                       | 35 |
| <b>Figure 84.</b> | EMI measurements for $20\text{ V}$ output profile, Line scan ( $115\text{ V}_{AC}$ ) . . . . .                          | 36 |
| <b>Figure 85.</b> | EMI measurements for $20\text{ V}$ output profile, Line scan ( $230\text{ V}_{AC}$ ) . . . . .                          | 36 |
| <b>Figure 86.</b> | EMI measurements for $20\text{ V}$ output profile, Neutral scan ( $115\text{ V}_{AC}$ ) . . . . .                       | 36 |
| <b>Figure 87.</b> | EMI measurements for $20\text{ V}$ output profile, Neutral scan ( $230\text{ V}_{AC}$ ) . . . . .                       | 36 |

**IMPORTANT NOTICE – PLEASE READ CAREFULLY**

STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST's terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers' products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. For additional information about ST trademarks, please refer to [www.st.com/trademarks](http://www.st.com/trademarks). All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2020 STMicroelectronics – All rights reserved