

STEVAL-ISA111V1: 12 V / 12 W, 115 kHz non-isolated flyback

By Mirko Sciortino

Introduction

This document describes a 12 V - 1 A power supply set in non-isolated flyback topology based on the VIPER26, an offline high-voltage converter offered by STMicroelectronics.

The features of the device include:


- 800 V avalanche rugged power section
- PWM operation at 115 kHz with frequency jittering for lower EMI
- Limiting current with adjustable set point
- On-board soft-start
- Safe behavior during a fault condition (overload, short-circuit, open loop)
- Low standby consumption (< 30 mW at $V_{IN} = 230$ V_{AC})

The available protections are:

- Thermal shutdown with hysteresis
- Delayed overload (or short-circuit) protection
- Open loop failure protection

All protections employ the auto-restart mode.

Figure 1. STEVAL-ISA111V1 evaluation board

 

Contents

1	Adapter features	4
2	Circuit description	5
3	Bill of material	8
4	Transformer	10
5	Testing the board	11
5.1	Typical waveforms	11
6	Line/load regulation and output voltage ripple	12
7	Burst mode and output voltage ripple	14
8	Efficiency	16
9	Light-load performance	17
10	Functional check	20
10.1	Soft-start	20
10.2	Overload protection	20
10.3	Feedback loop failure protection	21
11	Feedback loop calculation guidelines	23
11.1	Transfer function	23
11.2	Compensation procedure	24
12	Thermal measurements	26
13	EMI measurements	27
14	Board layout	29
15	Conclusions	30

**Appendix A Test equipment and measurement of efficiency
and light load performance. 31**

 A.1 Measuring input power 31

16 References 34

17 Revision history 35

1 Adapter features

The electrical specifications of the evaluation board are listed in [Table 1](#).

Table 1. Electrical specifications

Symbol	Parameter	Value
V_{IN}	Input voltage range	[90 V _{AC} - 265 V _{AC}]
V_{OUT}	Output voltage	12 V
I_{OUT}	Max. output current	1 A
ΔV_{OUT_LF}	Precision of output regulation	± 5%
ΔV_{OUT_HF}	High-frequency output voltage ripple	50 mV
T_{AMB}	Max. ambient operating temperature	60 °C

2 Circuit description

The power supply is set in flyback topology. The complete schematic is given in [Figure 2](#). A simplified schematic for $V_{OUT} \geq 12$ V and the relevant BOM are given in [Figure 3](#) and in [Table 2](#) respectively. The input section includes a resistor R1 and an NTC for inrush current limiting, a diode bridge (D0) and a Pi filter for EMC suppression (C1, L2, C2). The transformer core is a standard E20. A Transil™ clamp network (D1, D4) is used for leakage inductance demagnetization. The output voltage value is set simply through the R3-R4 voltage divider between the output terminal and the FB pin, according to the following formula:

Equation 1


$$V_{OUT} = 3.3V \cdot \left(1 + \frac{R3}{R4}\right)$$

In fact, the FB pin is the input of an error amplifier and is an accurate 3.3 V voltage reference. In the schematic the resistor R4 has been split into R4a and R4b in order to allow better tuning of the output voltage value. The compensation network is connected between the COMP pin (which is the output of the error amplifier) and the GND pin and consists of C7, C8 and R7. The output rectifier D3 has been selected according to the calculated maximum reverse voltage, forward voltage drop and power dissipation and is a power Schottky. A resistor has been connected between the LIM and GND pins in order to reduce the IDLIM to the value needed to supply the required output power, limiting the stress on the power components.

At power-up the DRAIN pin supplies the internal HV startup current generator which charges the VDD capacitor, C4, up to V_{DDon} . At this point, the Power MOSFET starts switching, the generator is turned off and the IC is powered by the energy stored in C4. If the nominal value of V_{OUT} exceeds the V_{DDcson} threshold of the VIPER26 by a small signal diode forward voltage drop, the IC can be supplied directly from the output, selecting jumper J2 which is shown as open in [Figure 2](#) (ie. no selection of either jumper J1 or J2 is indicated). In this case jumper J1 is open because the auxiliary winding of the transformer is not needed and the schematic can be simplified, as shown in [Figure 3](#). Since $V_{DDcsonmax} = 11.5$ V, the minimum value of V_{OUT} allowing this connection is 12 V. If $V_{OUT} < 12$ V, the VIPER26 must be supplied through the auxiliary winding of the transformer (J1 selected, J2 open in [Figure 2](#)), delivering to the VDD pin a voltage higher than V_{DDcson} . The voltage generated by the auxiliary winding increases with the load on the regulated output. An external clamp (D5, R1) can be added in this case, in order to avoid exceeding the V_{DD} operating range.

The figures and measurements in this document refer to a case in which V_{DD} is supplied from the output, i.e. to the simplified schematic shown in [Figure 3](#).


Figure 2. Application schematic - complete

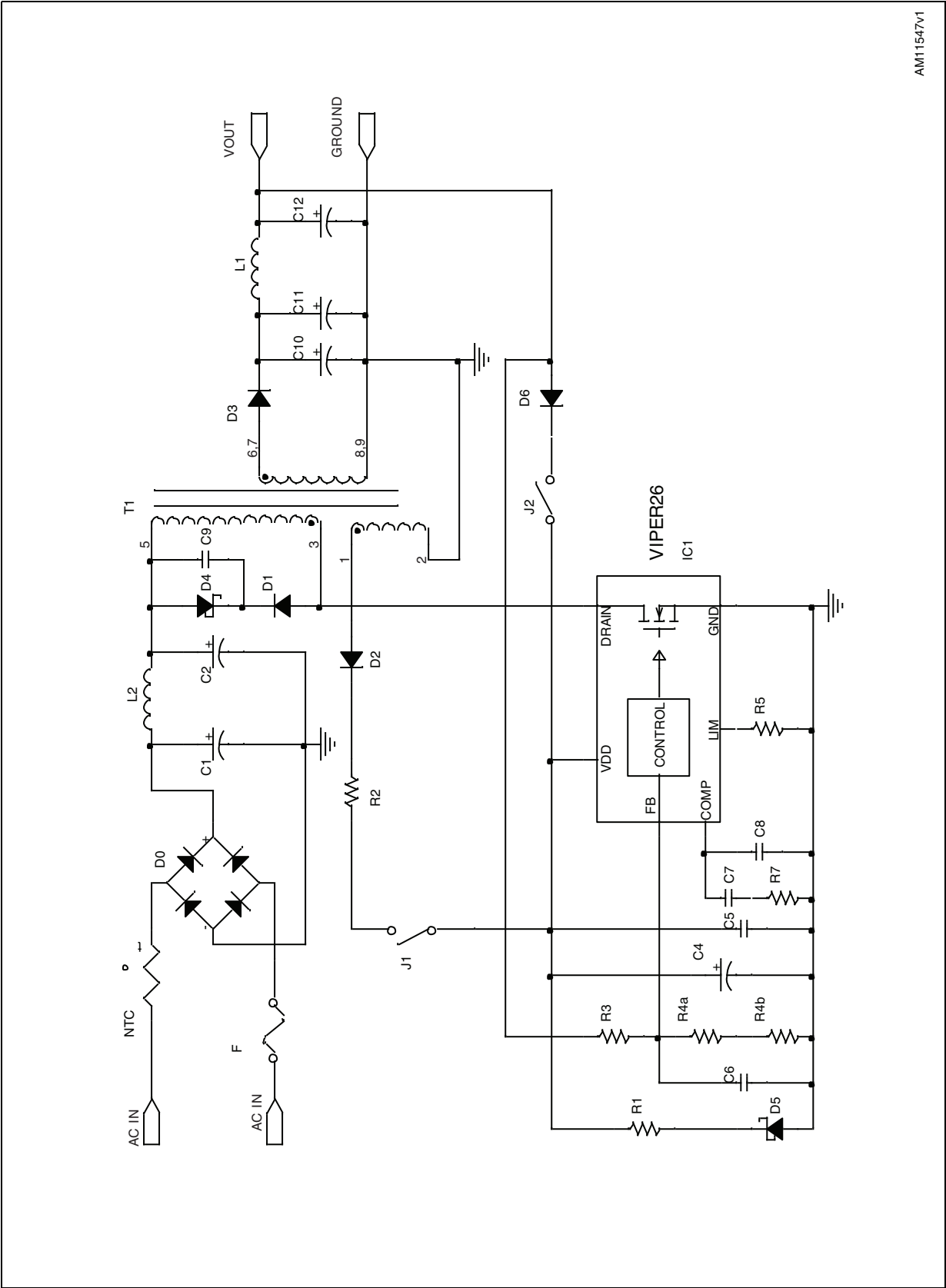

AM11547V1



Figure 3. Application schematic - simplified for $V_{OUT} \geq 12\text{ V}$

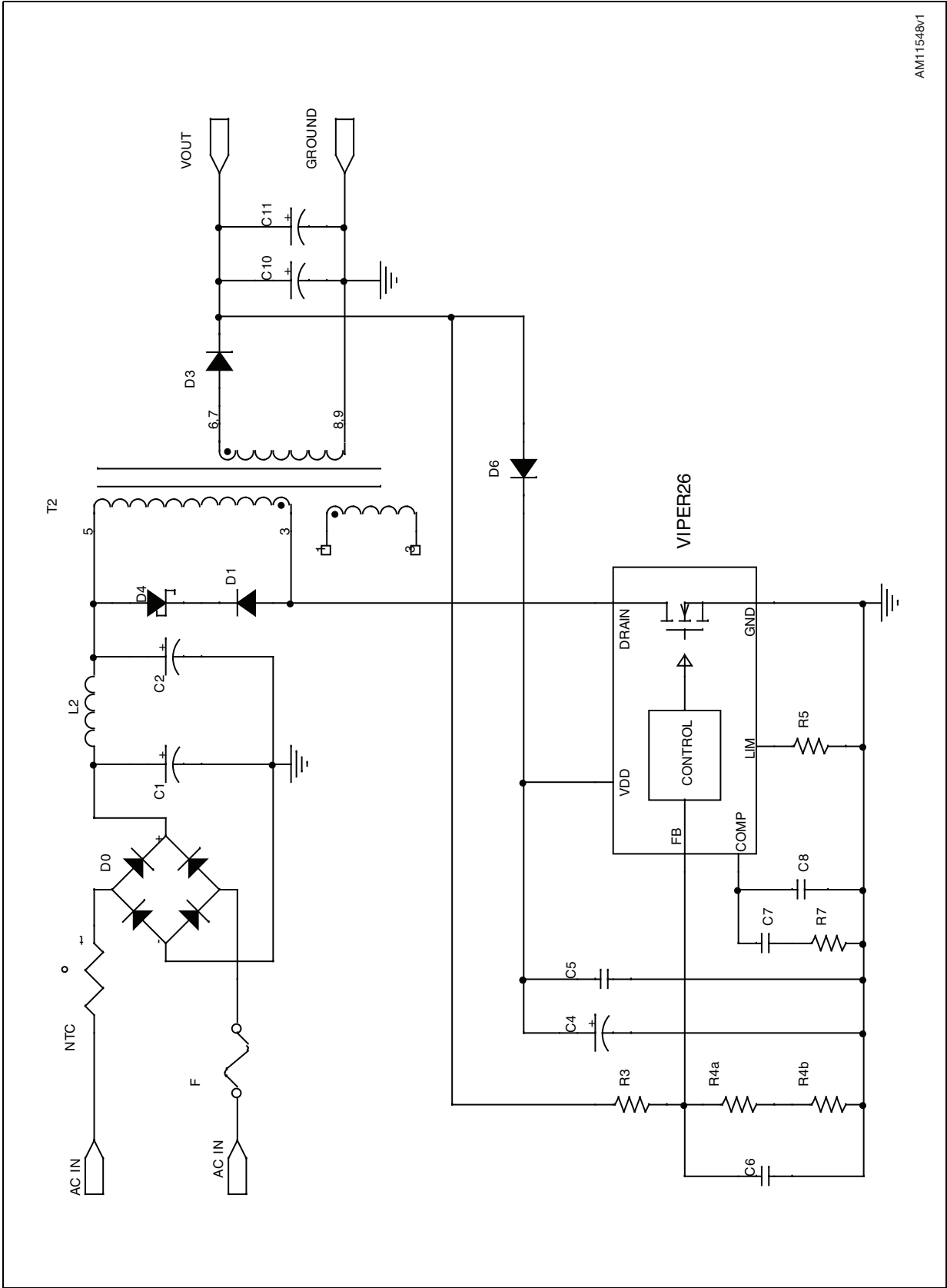

AM11548v1

3 Bill of material

Table 2. Bill of material (simplified schematic)

Reference	Part	Description	Manufacturer
NTC	2.2 Ω NTC	Thermistor, S236 series	EPCOS
F	T2A 250 V	2 A, 250 V _{AC} fuse, TR5 series	Wickmann
C1		10 μ F, 400 V NHG series electrolytic capacitor	Panasonic
C2		22 μ F, 35 V SMG series electrolytic capacitor	Panasonic
C4		2.2 μ F, 63 V electrolytic capacitor	
C5		100 nF, 50 V ceramic capacitor	
C6		2.2 nF, 50 V ceramic capacitor	
C7		100 nF, 50 V ceramic capacitor	
C8		2.2 nF, 50 V ceramic capacitor	
C9	Not mounted		
C10		1000 μ F, 16 V ultra low ESR electrolytic capacitor ZL series	Rubycon
C11		680 μ F, 16 V ultra low ESR electrolytic capacitor ZL series	Rubycon
C12	Not mounted		
D0	DF06M	1 A - 600 V diode bridge	Vishay
D1	STTH1L06	1 A - 600 V ultrafast diode	ST
D2	Not mounted		
D3	STPS3150	3 A-150 V power Schottky (output diode)	ST
D4	1.5KE300A	Transil	ST
D5	Not mounted		
D6	1N4148	Small signal diode	Fairchild
R1	Not mounted		
R2	Not mounted		
R3		47 k Ω 1% 1/4 W resistor	
R4a		15 k Ω 1% 1/4 W resistor	
R4b		2.7 k Ω 1% 1/4 W resistor	
R5		27 k Ω 1/4 W resistor	
R7		33 k Ω 1/4 W resistor	
L1	Short-circuit		
L2	RFB0807-102	Input filter inductor (L = 1 mH, I _{SAT} = 0.3 A; DCR _{max} = 3.4 Ω)	Coilcraft
T1	1335.0089	115 kHz switch mode transformer	Magnetica
	750810131 Rev. 6A	Flyback transformer	Würth
IC1	VIPER26HN	High-voltage 115 kHz PWM	ST

Table 2. Bill of material (simplified schematic) (continued)

Reference	Part	Description	Manufacturer
J1	Not mounted	Jumper	
J2	Short-circuit	Jumper	

4 Transformer

The characteristics of the transformer are listed in the table below.

Table 3. Transformer characteristics

Parameter	Value	Test conditions
Manufacturer	Magnetica	
Part number	1335.0089	
Primary inductance	1.8 mH \pm 15%	Measured at 1 kHz, T _{AMB} = 20 °C
Leakage inductance	3.12%	Measured at 10 kHz, T _{AMB} = 20 °C
Primary to secondary turn ratio (3 - 5)/(6,7- 8,9)	5.8 \pm 5%	Measured at 10 kHz, T _{AMB} = 20 °C
Primary to auxiliary turn ratio (3 - 5)/(1 - 2)	5.8 \pm 5%	Measured at 10 kHz, T _{AMB} = 20 °C

The figures below show the size, pinout, and pin distances (in mm) as well as the electrical diagram of the transformer.

Figure 4. Transformer size and pin diagram, bottom view

 


Figure 5. Transformer size, side view

 


Figure 6. Transformer, pin distances


 


Figure 7. Transformer, electrical diagram

 


5 Testing the board


5.1 Typical waveforms

Drain voltage and current waveforms in full load condition are shown for the two nominal input voltages in [Figure 8](#) and [9](#), and for minimum and maximum input voltage in [Figure 10](#) and [11](#) respectively.


**Figure 8. Drain current and voltage at $V_{IN} = 115$
 V_{AC} , full load**

 


**Figure 9. Drain current and voltage at $V_{IN} = 230$
 V_{AC} , full load**

 

**Figure 10. Drain current and voltage at $V_{IN} = 90$
 V_{AC} , full load**

 

**Figure 11. Drain current and voltage at $V_{IN} = 265$
 V_{AC} , full load**

 

6 Line/load regulation and output voltage ripple

The output voltage of the board has been measured in different line and load conditions. The results are shown in [Table 4](#). The output voltage is practically unaffected by the line condition.

Table 4. Output voltage line-load regulation

V_{IN} [V _{AC}]	V_{OUT} [V]			
	No load	50% load	75% load	100% load
90	11.94	11.91	11.92	11.92
115	11.94	11.91	11.92	11.92
150	11.94	11.92	11.91	11.91
180	11.94	11.92	11.91	11.91
230	11.94	11.92	11.91	11.91
265	11.94	11.92	11.91	11.91

Figure 12. Line regulation


 


Figure 13. Load regulation

 

The ripple at the switching frequency superimposed at the output voltage has also been measured and the results are given in [Table 5](#).

Table 5. Output voltage ripple at half and full load

V_{IN} [V _{AC}]	V_{OUT} [mV]	
	Half load	Full load
90	17	23
115	16	21
230	18	25
265	17	24

Figure 14. Output voltage ripple at $V_{IN} = 115\text{ V}_{AC}$, full load


 


Figure 15. Output voltage ripple at $V_{IN} = 230\text{ V}_{AC}$, full load

 

7 Burst mode and output voltage ripple

When the converter is lightly loaded, the COMP pin voltage decreases. As it reaches the shutdown threshold, V_{COMPL} (1.1 V, typical), the switching is disabled and energy is no longer transferred to the secondary side. So, the output voltage decreases and the regulation loop makes the COMP pin voltage increase again. As it rises 40 mV above the V_{COMPL} threshold, the normal switching operation is resumed. This results in a controlled on/off operation (referred to as "burst mode") as long as the output power is low enough to require a turn-on time lower than the minimum turn-on time of the VIPER26. This mode of operation keeps the frequency-related losses low when the load is very light or disconnected, making it easier to comply with energy-saving regulations. The figures below show the output voltage ripple when the converter is not (or lightly) loaded and supplied with 115 V_{AC} and with 230 V_{AC} respectively.

Figure 16. Output voltage ripple at $V_{\text{IN}} = 115 V_{\text{AC}}$, no load

 


Figure 17. Output voltage ripple at $V_{\text{IN}} = 230 V_{\text{AC}}$, no load

 


Figure 18. Output voltage ripple at $V_{\text{IN}} = 115 V_{\text{AC}}$, $I_{\text{OUT}} = 25 \text{ mA}$


 


Figure 19. Output voltage ripple at $V_{\text{IN}} = 230 V_{\text{AC}}$, $I_{\text{OUT}} = 25 \text{ mA}$

 

[Table 6](#) shows the measured value of the burst mode frequency ripple measured under different operating conditions. The ripple in burst mode operation is very low.

Table 6. Output voltage ripple at no (or light) load

V_{IN} [V _{AC}]	V_{OUT} [mV]	
	No load	25 mA load
90	2	3
115	2	5
230	2	6
265	3	6

8 Efficiency

Active mode efficiency is defined as the average of the efficiencies measured at 25%, 50%, 75% and 100% of maximum load, at nominal input voltage ($V_{IN} = 115 V_{AC}$ and $V_{IN} = 230 V_{AC}$).


External power supplies (the power supplies which are housed separately from the end-use devices they are powering) need to comply with the Code of Conduct (version 4.0) "Active mode efficiency" criterion, which requires an active mode efficiency higher than 77.7% for a power throughput of 12 W.

Another standard to be applied to external power supplies in the coming years is the DOE (Department of Energy) recommendation, whose active mode efficiency requirement for the same power throughput is 82.96%.

The average efficiencies of the board at 115 V_{AC} (83.33%) and at 230 V_{AC} (81.34%) are represented by dotted lines, and, along with the above limits, show that the STEVAL-ISA111V1 evaluation board is compliant with both standards at 115 V_{AC} and with the Code of Conduct only at 230 V_{AC} (refer to [Figure 20](#) below).

In the same figure the efficiency at 25%, 50%, 75% and 100% of maximum load for both input voltages is also shown.

Figure 20. Active mode efficiency of the evaluation board in comparison to energy efficiency standards

 

9 Light-load performance

The input power of the converter has been measured in no load condition for different input voltages and the results are given in [Table 7](#).

Table 7. No load input power

V_{IN} [V _{AC}]	P_{IN} [mW]
90	13.4
115	14.4
150	16.1
180	18.0
230	22.2
265	24.9

In version 4.0 of the Code of Conduct the power consumption of the power supply when it is not loaded is also considered. The criteria for compliance are given in the table below:

Table 8. Energy consumption criteria for no load

Nameplate output power (P_{no})	Maximum power in no load for AC-DC EPS
$0\text{ W} \leq P_{no} \leq 50\text{ W}$	$< 0.3\text{ W}$
$50\text{ W} < P_{no} < 250\text{ W}$	$< 0.5\text{ W}$

The power consumption of the STEVAL-ISA111V1 board is about ten times lower than the Code of Conduct (version 4) limit. Even if this performance seems to be disproportionately better than the requirements, it is worth noting that often AC-DC adapter or battery charger manufacturers have very strict requirements about no load consumption and when the converter is used as an auxiliary power supply, the line filter is often the main line filter of the entire power supply which considerably increases standby consumption.

Even if the Code of Conduct (version 4) program does not have other requirements regarding light load performance, in order to give more information the input power and efficiency of the evaluation board in two other light load cases is also shown. [Table 9](#) and [Table 10](#) show the performance when the output load is 25 mW and 50 mW respectively.

Table 9. Light load performance at $P_{OUT} = 25\text{ mW}$

V_{IN} [V _{AC}]	P_{OUT} [mW]	P_{IN} [mW]	Efficiency (%)
90	25	44.9	55.7
115	25	46.3	54.0
150	25	49.1	50.9
180	25	51.5	48.5


Table 9. Light load performance at $P_{OUT} = 25 \text{ mW}$

$V_{IN} [V_{AC}]$	$P_{OUT} [mW]$	$P_{IN} [mW]$	Efficiency (%)
230	25	55.0	45.5
265	25	59.0	42.4

Table 10. Light load performance at $P_{OUT} = 50 \text{ mW}$

$V_{IN} [V_{AC}]$	$P_{OUT} [mW]$	$P_{IN} [mW]$	Efficiency (%)
90	50	76.7	65.2
115	50	78.5	63.7
150	50	82.0	61.0
180	50	85.0	58.8
230	50	90.0	55.6
265	50	94.0	53.2


The input power vs. input voltage for no load and light load condition ([Table 7](#), [9](#) and [10](#)) are shown in the figure below.

  Figure 21. P_{IN} vs. V_{IN} at no load and light load

 
It's possible to have several criteria to measure the standby or light load performance of a converter. One criterion is the measurement of the output power when the input power is equal to one watt. In [Table 11](#) the output power needed to have 1 W of input power in different line conditions is given. [Figure 22](#) shows the output power corresponding to $P_{IN} = 1 \text{ W}$ for different values of the input voltage.

Table 11. P_{OUT} @ $P_{IN} = 1\text{ W}$

V_{IN} [V _{AC}]	P_{IN} (W)	P_{OUT} (W)	Efficiency (%)
90	1	0.788	78.8
115	1	0.781	78.1
150	1	0.76	76.0
180	1	0.74	74.0
230	1	0.70	70.0
265	1	0.686	68.6

Figure 22. Efficiency vs. V_{IN} at $P_{IN} = 1\text{ W}$ 

Another requirement (EuP lot 6) is that the input power should be less than 500 mW when the converter is loaded with 250 mW. The converter can satisfy even this requirement, as shown in [Figure 23](#).

Figure 23. P_{IN} at $P_{OUT} = 0.25\text{ W}$ 

10 Functional check

10.1 Soft-start

At startup the current limitation value reaches IDLIM after an internally set time, t_{SS} , whose typical value is 8.5 msec. This time is divided into 16 time intervals, each corresponding to a current limitation step progressively increasing. In this way the drain current is limited during the output voltage increase, therefore reducing the stress on the secondary diode. The soft-start phase is shown in [Figure 24](#) and [25](#).

Figure 24. Soft-start at startup


 


Figure 25. Soft-start at startup (zoom)

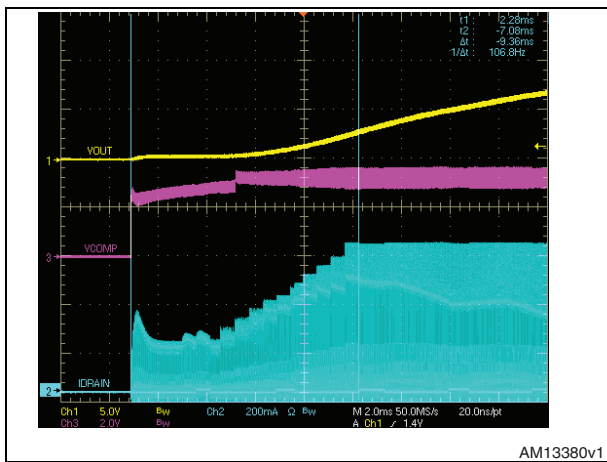

10.2 Overload protection

In case of overload or short-circuit (see [Figure 26](#)), the drain current reaches the IDLIM value (or the one set by the user through the RLIM resistor). Every cycle that this condition is met, a counter is incremented. If the fault is maintained continuously for the time t_{OVL} (50 msec typical, set internally), the overload protection is tripped, the power section is turned off and the converter is disabled for a $t_{RESTART}$ time (1 s typical). After this time has elapsed, the IC resumes switching and, if the short is still present, the protection occurs indefinitely in the same way ([Figure 27](#)). This ensures restart attempts of the converter with low repetition rate, so that it works safely with extremely low power throughput and avoids overheating of the IC in case of repeated overload events.

Moreover, every time the protection is tripped, the internal soft-start function ([Figure 25](#)) is implemented, in order to reduce the stress on the secondary diode.

After the short removal, the IC resumes working normally. If the short is removed during t_{SS} or t_{OVL} , i.e. before the protection is tripped, the counter is decremented on a cycle-by-cycle basis down to zero and the protection is not tripped.

If the short-circuit is removed during $t_{RESTART}$, the IC waits for the $t_{RESTART}$ period to elapse before resuming switching ([Figure 29](#)).

Figure 26. Output short-circuit applied:
OLP tripping

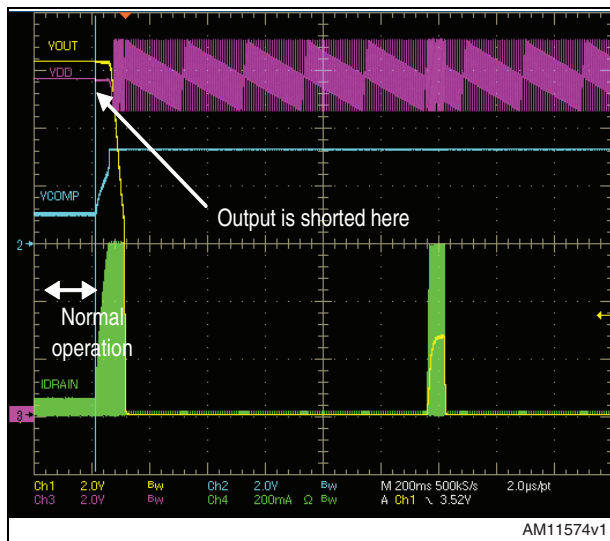


Figure 27. Output short-circuit maintained: OLP
steady-state

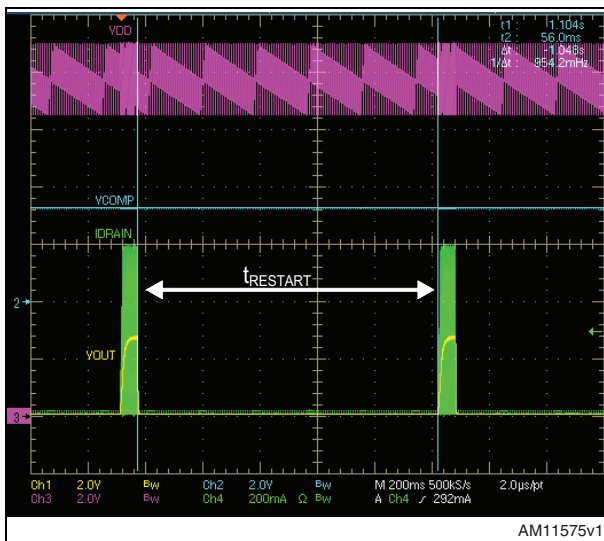


Figure 28. Output short-circuit maintained: OLP
steady-state, zoom


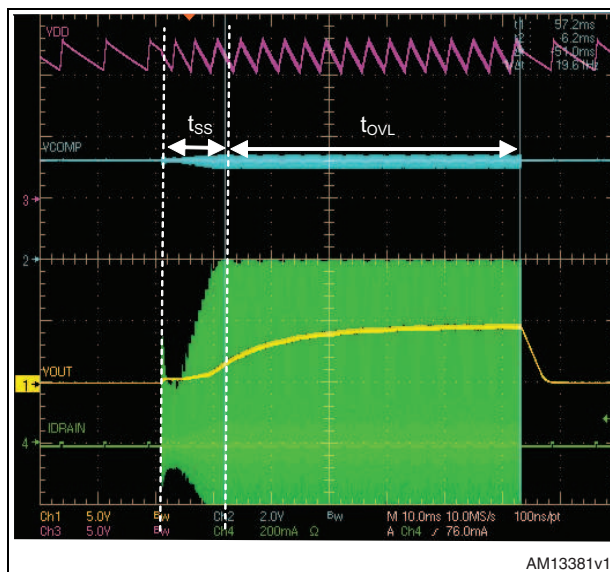


Figure 29. Output short-circuit removal and
converter restart

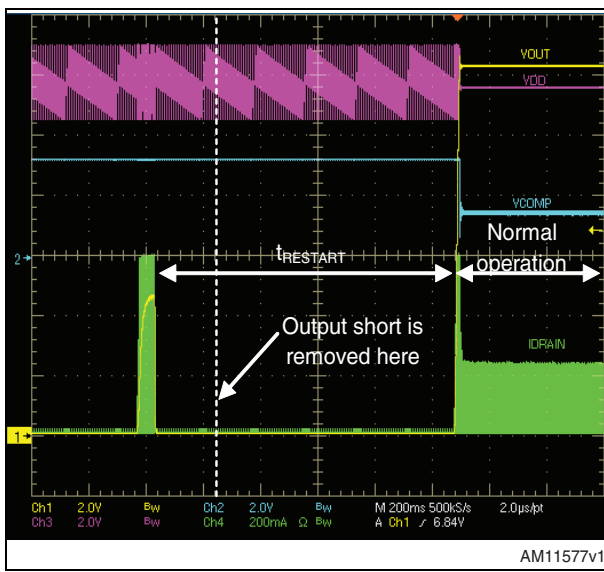

10.3 Feedback loop failure protection

When the loop is broken ($R4 = R4a + R4b$ shorted or $R3$ open), the output voltage V_{OUT} increases and the VIPER26 runs at its maximum current limitation. The V_{DD} pin voltage increases as well, because it is linked to the V_{OUT} voltage either directly or through the auxiliary winding.

If the V_{DD} voltage reaches the $V_{DDclamp}$ threshold (23.5 V min.) in less than 50 msec, the IC is shut down by the open loop failure protection (see [Figure 30](#) and [31](#)), otherwise by OLP, as described in the previous section. The breaking of the loop has been simulated by

shorting the low-side resistor of the output voltage divider, $R4 = R4a + R4b$. The same behavior can be caused by opening the high-side resistor, $R3$.

The protection acts in auto-restart mode with $t_{\text{RESTART}} = 1 \text{ s}$ (Figure 31). When the fault is removed, normal operation is restored after the last t_{RESTART} interval has been completed (Figure 33).

Figure 30. Feedback loop failure protection: tripping

 


Figure 31. Feedback loop failure protection: steady-state

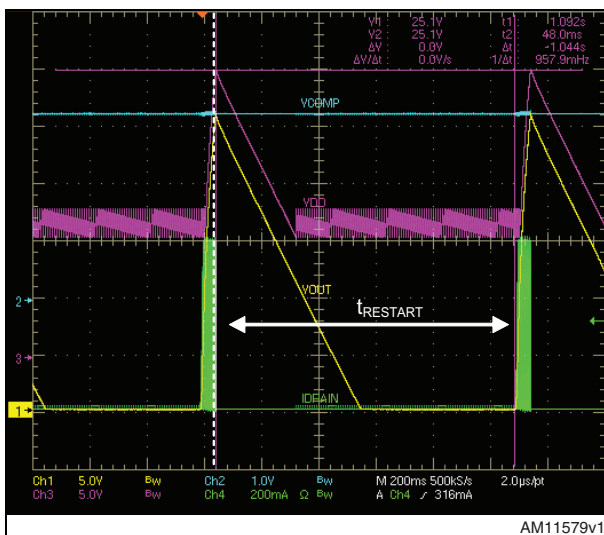


Figure 32. Feedback loop failure protection: steady-state, zoom


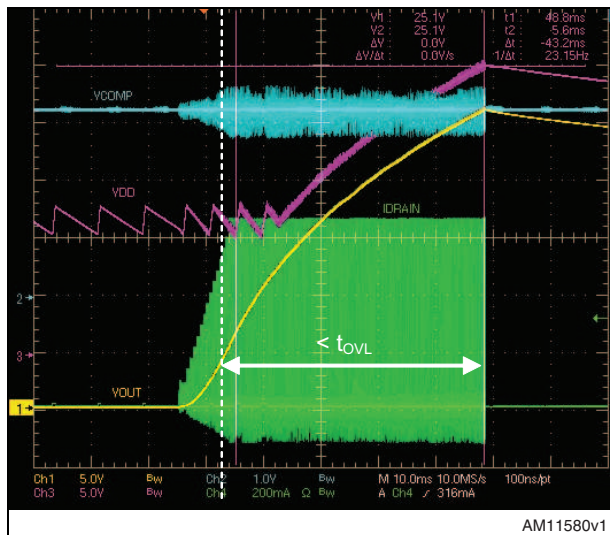


Figure 33. Feedback loop failure removal: converter restart

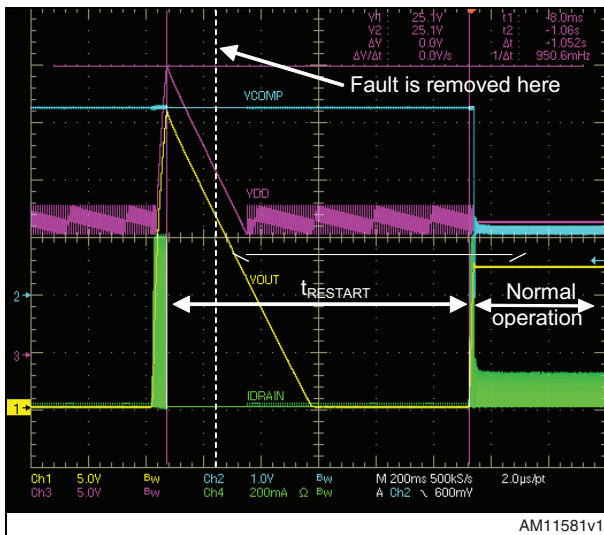


11 Feedback loop calculation guidelines

11.1 Transfer function

The set PWM modulator + power stage is indicated with $G_1(f)$, while $C(f)$ is the “controller”, i.e. the network which is in charge of ensuring the stability of the system.

Figure 34. Control loop block diagram

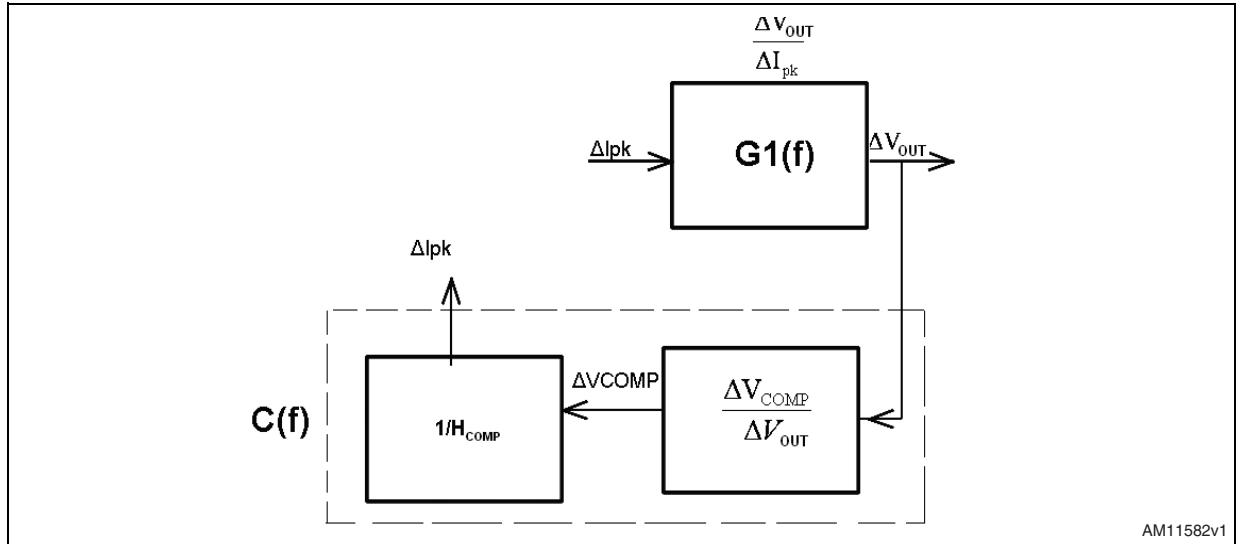

The mathematical expression of the power plant $G_1(f)$ is the following:

Equation 2

$$G_1(f) = \frac{\Delta V_{OUT}}{\Delta I_{pk}} = \frac{V_{OUT} \cdot (1 + \frac{j \cdot 2 \cdot \pi \cdot f}{z})}{I_{pkp}(f_{sw}, V_{dc}) \cdot (1 + \frac{j \cdot 2 \cdot \pi \cdot f}{p})} = \frac{V_{OUT} \cdot (1 + \frac{j \cdot f}{f_z})}{I_{pkp}(f_{sw}, V_{dc}) \cdot (1 + \frac{j \cdot f}{f_p})}$$

where V_{OUT} is the output voltage, I_{pkp} is the primary peak current, f_p is the frequency of the pole due to the output load:

Equation 3

$$f_p = \frac{1}{\pi \cdot C_{OUT} \cdot (R_{OUT} + 2ESR)}$$

and f_z the frequency of the zero due to the ESR of the output capacitor:

Equation 4

$$f_z = \frac{1}{2 \cdot \pi \cdot C_{OUT} \cdot ESR}$$

The mathematical expression of the compensator $C(f)$ is:

Equation 5

$$C(f) = \frac{\Delta I_{pk}}{\Delta V_{OUT}} = \frac{C_0}{H_{COMP}} \cdot \frac{1 + \frac{f \cdot j}{fZc}}{2 \cdot \pi \cdot f \cdot j \cdot \left(1 + \frac{f \cdot j}{fPc}\right)}$$

where (with reference to the schematic of [Figure 2](#)):

Equation 6

$$C_0 = -\frac{Gm}{C7 + C8} \cdot \frac{R4}{R3 + R4}$$

Equation 7

$$fZc = \frac{1}{2 \cdot \pi \cdot R7 \cdot C7}$$

Equation 8

$$fPc = \frac{C7 + C8}{2 \cdot \pi \cdot R7 \cdot C7 \cdot C8}$$

are to be chosen with the purpose to ensure the stability of the overall system. $Gm = 2 \text{ mA/V}$ (typical) is the VIPER26 transconductance.

11.2 Compensation procedure

The first step is to choose the pole and zero of the compensator and the crossover frequency, for instance:

- $fZc = fp/2$
- $fPc = fz$
- $fcross = fcross_sel \leq fsw/10$.

$G1(fcross_sel)$ can be calculated from [Equation 2](#) and, being by definition $|C(fcross_sel) \cdot G1(fcross_sel)| = 1$, C_0 can be calculated as follows:

Equation 9

$$C_0 = \frac{\left| 2 \cdot \pi \cdot fcross_sel \cdot j \right| \cdot \left| 1 + \frac{fcross_sel \cdot j}{fPc} \right|}{\left| 1 + \frac{fcross_sel \cdot j}{fZc} \right|} \cdot \frac{H_{COMP}}{\left| G1(fcross_sel) \right|}$$

At this point the Bode diagram of $G_1(f) \cdot C(f)$ can be plotted, in order to check the phase margin for the stability. If the margin is not high enough, another choice should be made for f_{Zc} , f_{Pc} and f_{cross_sel} , and the procedure repeated. When the stability is ensured, the next step is to find the values of the schematic components, which can be calculated using [Equation 1](#), [6](#), [7](#), [8](#), [9](#) as follows:

Equation 10

$$R4 = \frac{R3}{\frac{V_{OUT}}{3.3V} - 1}$$

Equation 11

$$C8 = \frac{f_{Zc}}{f_{Pc}} \cdot \frac{Gm}{|C0|} \cdot \frac{R4}{R4 + R3}$$

Equation 12

$$C7 = C8 \cdot \left(\frac{f_{Pc}}{f_{Zc}} - 1 \right)$$

Equation 13

$$R7 = \frac{C7 + C8}{2 \cdot \pi \cdot f_{Pc} \cdot C7 \cdot C8}$$

12 Thermal measurements

A thermal analysis of the board at full load condition, @ $T_{AMB} = 25\text{ }^{\circ}\text{C}$ has been performed using an IR camera. The worst case is $V_{IN} = 85\text{ V}_{AC}$, but the nominal input voltage cases ($V_{IN} = 115\text{ V}_{AC}$ and $V_{IN} = 230\text{ V}_{AC}$) have also been considered. The results are shown in [Figure 35](#), [36](#), [37](#) and [38](#) and summarized in [Table 12](#).

Figure 35. Thermal map at $T_{AMB} = 25\text{ }^{\circ}\text{C}$, $V_{IN} = 85\text{ V}_{AC}$, full load

 


Figure 36. Thermal map at $T_{AMB} = 25\text{ }^{\circ}\text{C}$, $V_{IN} = 115\text{ V}_{AC}$, full load

 


Figure 37. Thermal map at $T_{AMB} = 25\text{ }^{\circ}\text{C}$, $V_{IN} = 230\text{ V}_{AC}$, full load

 


Figure 38. Thermal map at $T_{AMB} = 25\text{ }^{\circ}\text{C}$, $V_{IN} = 265\text{ V}_{AC}$, full load

 


Table 12. Temperature of key components at $V_{IN} = 85\text{ V}_{AC}/230\text{ V}_{AC}$, full load ($T_{AMB} = 25\text{ }^{\circ}\text{C}$)

Point	T [$^{\circ}\text{C}$]		Reference
	$V_{IN} = 85\text{ V}_{AC}$	$V_{IN} = 265\text{ V}_{AC}$	
A	82.4	76.6	VIPER26
B	68.3	73.3	Transformer
C	69.1	67.0	Output diode
D	55.4	53.0	Clamping diode
E	24.8	24.9	Room temperature

13 EMI measurements

A pre-compliance test to EN55022 (Class B) European normative has been performed using an EMC analyzer and an LISN. First of all, a measurement of the background noise (board disconnected from the mains) was performed and is shown in [Figure 39](#).

Then the peak and average EMC measurements at 115 V_{AC}/full load and 230 V_{AC}/full load were performed and the results are shown in [Figure 40](#), [41](#), [42](#) and [43](#).

Figure 39. Background noise measurement

 


Figure 40. Peak measurement at 115 V_{AC}/full load

 


Figure 41. Peak measurement at 230 V_{AC}/full load

 


Figure 42. Average measurement at 115 V_{AC}/full load


 



Figure 43. Average measurement at 230 V_{AC}/full load

 

14 Board layout

The board layout is shown in the figure below.

Figure 44. Bottom layer & top overlay

 

AM11589v1

15 Conclusions


The VIPER26 allows a simple design of a non-isolated converter with few external components. In this document a non-isolated flyback has been described and characterized. Special attention has been given to light load performance, confirmed as very good by bench analysis. Efficiency has been compared to the requirements of the Code of Conduct (version 4) for external AC-DC power supplies with very good results.

Appendix A Test equipment and measurement of efficiency and light load performance

The converter input power has been measured using a wattmeter. The wattmeter measures simultaneously the converter input current (using its internal ammeter) and voltage (using its internal voltmeter). The wattmeter is a digital instrument so it samples the current and voltage and converts them to digital forms. The digital samples are then multiplied giving the instantaneous measured power. The sampling frequency is in the range of 20 kHz (or higher depending on the instrument used). The display provides the average measured power, averaging the instantaneous measured power in a short period of time (1 sec typ.).

Figure 45 shows how the wattmeter is connected to the UUT (unit under test) and to the AC source and the wattmeter internal block diagram.

Figure 45. Connections of the UUT to the wattmeter for power measurements

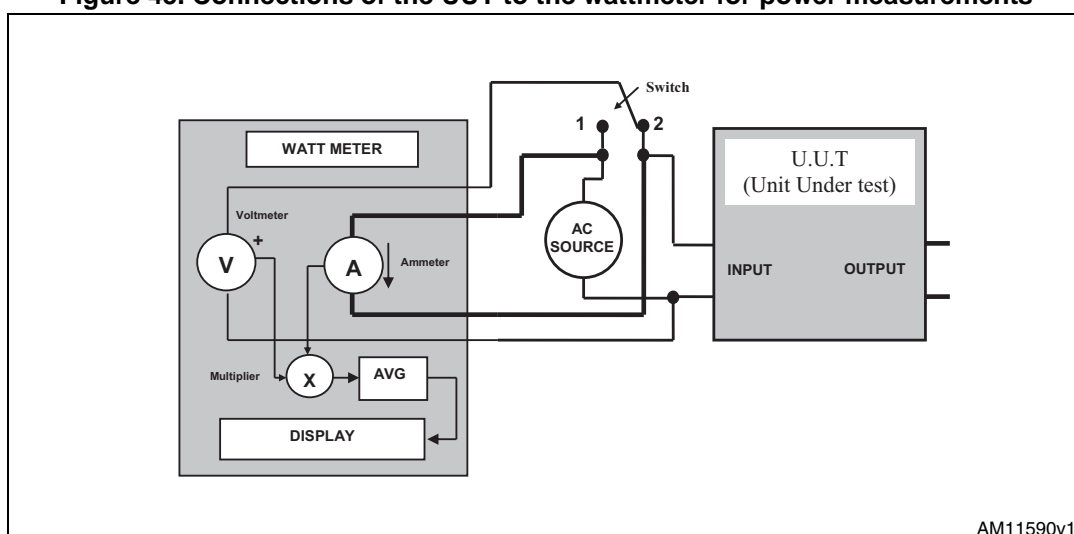


AM11590v1

An electronic load has been connected to the output of the power converter (UUT), allowing the converter load current to be set and measured, while the output voltage has been measured by a voltmeter. The output power is the product between load current and output voltage. The ratio between the output power, calculated as previously stated, and the input power, measured by the wattmeter, is the converter's efficiency, which has been measured in different input/output conditions.


A.1 Measuring input power

With reference to Figure 45, the UUT input current causes a voltage drop across the ammeter's internal shunt resistance (the ammeter is not ideal as it has an internal resistance higher than zero) and across the cables connecting the wattmeter to the UUT.

If the switch of Figure 45 is in position 1 (see also the simplified scheme of Figure 46), this voltage drop causes an input measured voltage higher than the input voltage at the UUT input that, of course, affects the measured power. The voltage drop is generally negligible if the UUT input current is low (for example when we are measuring the input power of UUT in light load condition).

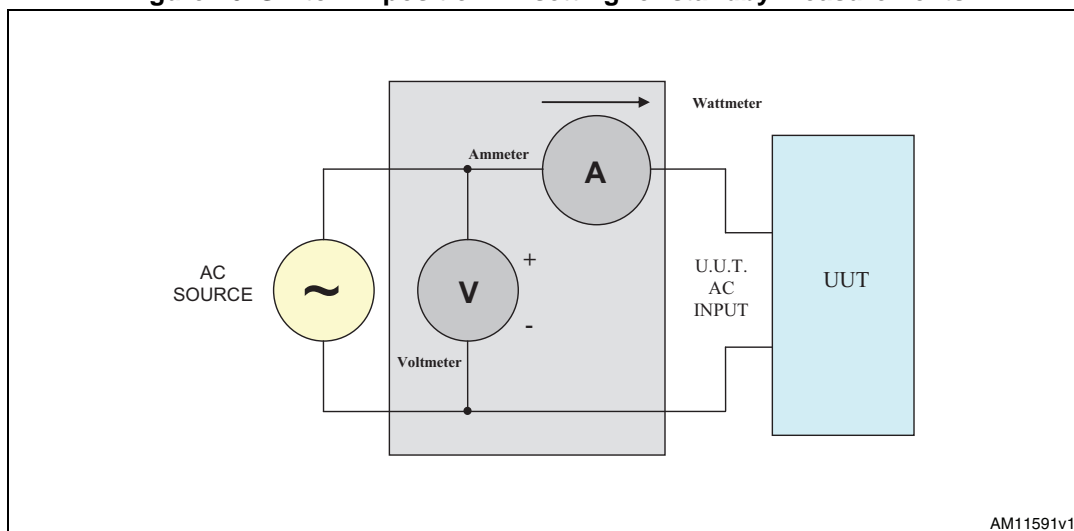Figure 46. Switch in position 1 - setting for standby measurements

In the case of high UUT input current (i.e. for measurements in heavy load conditions), the voltage drop can be relevant compared to the UUT real input voltage. If this is the case, the switch in [Figure 45](#) can be changed to position 2 (see simplified scheme of [Figure 47](#)) where the UUT input voltage is measured directly at the UUT input terminal and the input current does not affect the measured input voltage.

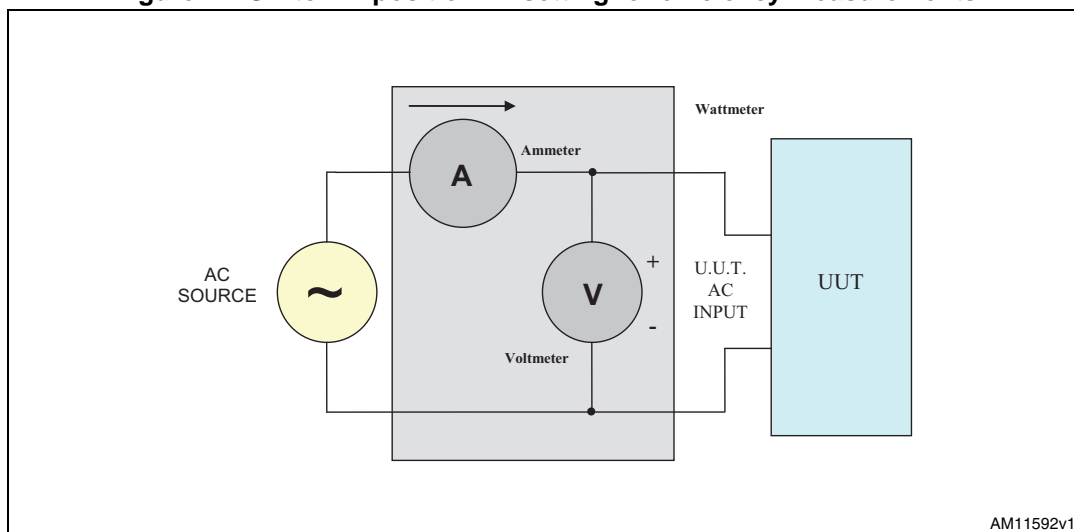Figure 47. Switch in position 2 - setting for efficiency measurements

On the other hand, the position of [Figure 47](#) may introduce a relevant error during light load measurements, when the UUT input current is low and the leakage current inside the voltmeter itself (which is not an ideal instrument and doesn't have infinite input resistance) is not negligible. This is the reason why it is better to use the setting of [Figure 46](#) for light load measurements and [Figure 47](#) for heavy load measurements.

If it is not clear which measurement scheme has the lesser effect on the result, try with both and register the lower input power value.

As noted in IEC 62301, instantaneous measurements are appropriate when power readings are stable. The UUT is operated at 100% of nameplate output current output for at least 30 minutes (warm-up period) immediately prior to conducting efficiency measurements.

After this warm-up period, the AC input power is monitored for a period of 5 minutes to assess the stability of the UUT. If the power level does not drift by more than 5% from the maximum value observed, the UUT can be considered stable and the measurements can be recorded at the end of the 5-minute period. If AC input power is not stable over a 5-minute period, the average power or accumulated energy is measured over time for both AC input and DC output.

Some wattmeter models allow integration of the measured input power in a time range and then measure the energy absorbed by the UUT during the integration time. The average input power is calculated dividing by the integration time itself.

16 References

- Code of Conduct on energy efficiency of external power supplies, version 4
- VIPER26 datasheet

17 Revision history

Table 13. Document revision history

Date	Revision	Changes
18-Feb-2013	1	Initial release.
18-May-2016	2	Added: new T1 part 750810131 Rev 6A in Table 2 .

IMPORTANT NOTICE – PLEASE READ CAREFULLY

STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST's terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers' products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2016 STMicroelectronics – All rights reserved