

DT0002 Design tip

Reducing torque variation in half step drive

By Thomas Hopkins

	Main components
L6506	Current Controller For Stepping Motors
L6207, L6227	Dual DMOS Full Bridge Driver with PWM Current Controller

Purpose and benefits

This note describes a technique to reduce torque variation when driving two phase bipolar stepper motors in half step. Reducing the torque variation can reduce the chance of the motor stalling and give more reliable operation.

Description

The stepping sequence for a half step drive of a two phase bipolar stepper motor alternates between states driving current in both phases and driving current in only one phase. In many implementations, the current level is set to be the same whether one or both phases of the motor are being driven, as shown in Figure 1a.

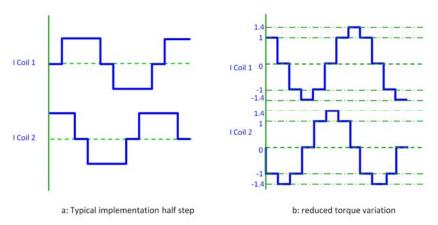


Figure 1. Current waveforms in half step operation

For the motor, torque is proportional to the magnitude of the stator and rotor magnetic vectors times the sine of the angle between the stator vector and the rotor vector. When driving a motor with two coils, the magnitude of the resulting magnetic vector is the vector sum of the vectors produced by each coil. If the two coils are oriented 90 degrees apart

April 2012 DT0002 Rev 1 1/3

and are driven with equal currents, the magnitude of the resulting magnetic vector is $\sqrt{2}$, or approximately 1.4, times the magnitude of the individual vectors. Since torque is proportional to the amplitude of this vector, one can easily see that as the magnitude of the vector changes from 1.4, with both coils energized, to 1, with only one coil energized, the torque also is changing and has a variation of about 40%.

This variation can be reduced by increasing the current in the coil during the half steps when only one coil is being driven. If the magnitude of the current is increased by $\sqrt{2}$, as shown in Figure 1b, the magnitude of the magnetic vector will also be increased by $\sqrt{2}$ and will be equal to the magnitude of the vector when both coils were driven by the original current.

Figure 2 shows an easy way to implement a circuit to drive the stepper as shown in Figure 1b. In this example, the microcontroller provides the phase and enable information for the stepper to a driver like the L6207 or L6227 or a current controller like the L6506 used with a driver IC like the L6201, L6202, L6203 or L298. The resistor values are calculated so that the reference voltage is reduced by a ratio of 1.4:1 when the open drain output is turned on. For a typical implementation, the values may be set at 0.7V and 0.5V. When the microcontroller turns both coils on, it also turns on the open drain device and reduces the

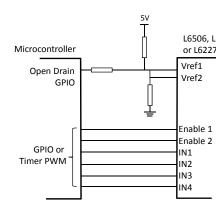


Figure 2. Connection Diagram

reference voltage. When only one coil is energized, the open drain device is turned off and the reference voltage is raised to the higher value so that the current in the single coil is increased to 1.4 times the current when both coils are on.

With this technique, the variation in torque caused by the one on - two on drive pattern can be reduced or eliminated.

Support material

Documentation		
Datasheet L6506, Current Controller For Stepping Motors		
Datasheet L6207, Dual DMOS Full Bridge Driver with PWM Current Controller		
Datasheet L6227, Dual DMOS Full Bridge Driver with PWM Current Controller		

Revision history

Date	Version	Changes
19-Apr-2012	1	Initial release

Please Read Carefully

Information in this document is provided solely in connection with ST products. STMicroelectronics NV and its subsidiaries ("ST") reserve the right to make changes, corrections, modifications or improvements, to this document, and the products and services described herein at any time, without notice.

All ST products are sold pursuant to ST's terms and conditions of sale.

Purchasers are solely responsible for the choice, selection and use of the ST products and services described herein, and ST assumes no liability whatsoever relating to the choice, selection or use of the ST products and services described herein.

No license, express or implied, by estoppel or otherwise, to any intellectual property rights is granted under this document. If any part of this document refers to any third party products or services it shall not be deemed a license grant by ST for the use of such third party products or services, or any intellectual property contained therein or considered as a warranty covering the use in any manner whatsoever of such third party products or services or any intellectual property contained therein

UNLESS OTHERWISE SET FORTH IN ST'S TERMS AND CONDITIONS OF SALE ST DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY WITH RESPECT TO THE USE AND/OR SALE OF ST PRODUCTS INCLUDING WITHOUT LIMITATION IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE (AND THEIR EQUIVALENTS UNDER THE LAWS OF ANY JURISDICTION), OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

UNLESS EXPRESSLY APPROVED IN WRITING BY TWO AUTHORIZED ST REPRESENTATIVES, ST PRODUCTS ARE NOT RECOMMENDED, AUTHORIZED OR WARRANTED FOR USE IN MILITARY, AIR CRAFT, SPACE, LIFE SAVING, OR LIFE SUSTAINING APPLICATIONS, NOR IN PRODUCTS OR SYSTEMS WHERE FAILURE OR MALFUNCTION MAY RESULT IN PERSONAL INJURY, DEATH, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. ST PRODUCTS WHICH ARE NOT SPECIFIED AS "AUTOMOTIVEGRADE" MAY ONLY BE USED IN AUTOMOTIVE APPLICATIONS AT USER'S OWN RISK.

Resale of ST products with provisions different from the statements and/or technical features set forth in this document shall immediately void any warranty granted by ST for the ST product or service described herein and shall not create or extend in any manner whatsoever, any liability of ST.

ST and the ST logo are trademarks or registered trademarks of ST in various countries.

Information in this document supersedes and replaces all information previously supplied.


The ST logo is a registered trademark of STMicroelectronics. All other names are the property of their respective owners.

© 2012 STMicroelectronics - All rights reserved

STMicroelectronics group of companies

Australia - Belgium - Brazil - Canada - China - Czech Republic - Finland - France - Germany - Hong Kong - India - Israel - Italy - Japan - Malaysia - Malta - Morocco - Philippines - Singapore - Spain - Sweden - Switzerland - United Kingdom - United States of America

www.st.com

 

www.st.com